

Ve270 Introduction to Logic Design

Homework 6

Assigned: June 22, 2017

Due: June 29, 2017, at the beginning of the class.

The homework should be submitted in hard copies.

1. Problem 4.2 (10 points)
- 4.2 Trace the behavior of an 8-bit parallel-load register with 8-bit input I , 8-bit output Q , load control input ld , and synchronous clear input clr by completing the timing diagram in Figure 4.96.

 


Figure 4.96

2. Problem 4.3, using components to draw schematic (20 points)
- 4.3 Design a 4-bit register with 2 control inputs $s1$ and $s0$; 4 data inputs $I3$, $I2$, $I1$, and $I0$; and 4 data outputs $Q3$, $Q2$, $Q1$, and $Q0$. When $s1s0=00$, the register maintains its value. When $s1s0=01$, the register loads $I3...I0$. When $s1s0=10$, the register clears itself to 0000. When $s1s0=11$, the register complements itself, so for example, 0000 would become 1111, and 1010 would become 0101. (*Component design problem.*)
3. Problem 4.46. Draw schematic. (20 Points).
- 4.46 Design a special multiplier circuit that can multiply its 16-bit input by 2, 4, 8, 16, or 32, specified by three inputs a , b , c ($abc=000$ means no multiply, $abc=001$ means multiply by 2, $abc=010$ means by 4, $abc=011$ means by 8, $abc=100$ means by 16, $abc=101$ means by 32). *Hint: A simple solution consists entirely of just one copy of a component from this chapter. (Component use problem.)*



4. Problem 4.57. Draw schematic (a), (b). (20 points)

4.57 Design a circuit that outputs a 1 every 99 clock cycles:

- (a) Using an up-counter with a synchronous clear control input, and using extra logic,
- (b) Using a down-counter with parallel load, and using extra logic.

5. Design a circuit called Receiver that receives two single bit signals, **Valid** and **Data_in**, from another device called Transmitter. The **Valid** signal sent from the Transmitter will be a 1-clock cycle pulse. The first bit of **Data_in** comes at the same time as **Valid**. Once the Receiver detects the **Valid** pulse, it will start receiving 8 bits through port **Data_in**, bit by bit. After the 8 bits of information is received, it should be copied into another 8-bit register called **RxReg**. Draw the schematic on component level (30 Points).