




# Topic 13

## RTL Design

---
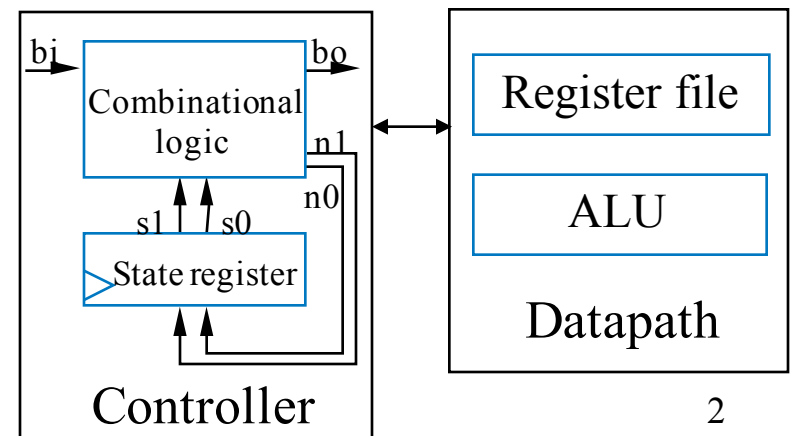 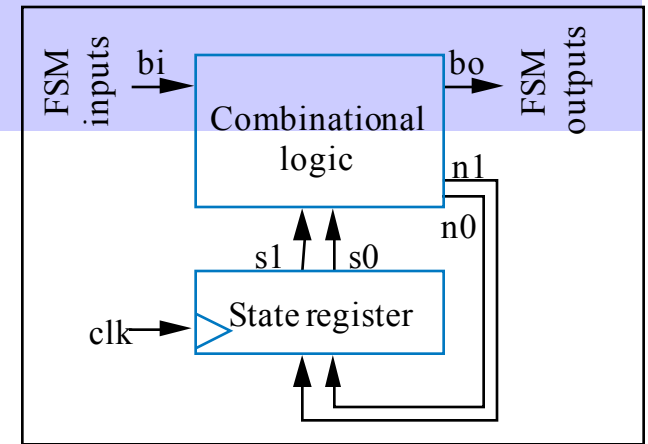
# Introduction

- **Controllers (FSM)**
  - Describes behavior of circuits
  - Takes inputs, generates outputs
  - Implemented with state register and combinational logic
- **Datapath components**
  - Operations on data
  - Path that data flows through
  - Places data is stored
- **Digital Device**
  - Controller and datapath components working together
  - To implement an algorithm
  - Design on Register Transfer Level




# RTL Design Method

Step	Description
Step 1 <i>Capture a high-level state machine</i>	Describe the system's desired behavior as a high-level state machine. The state machine consists of states and transitions. The state machine is "high-level" because the transition conditions and the state actions are more than just Boolean operations on bit inputs and outputs.
Step 2 <i>Create a datapath</i>	Create a datapath to carry out the data operations of the high-level state machine.
Step 3 <i>Connect the datapath to a controller</i>	Connect the datapath to a controller block. Connect external Boolean inputs and outputs to the controller block.
Step 4 <i>Derive the controller's FSM</i>	Convert the high-level state machine to a finite-state machine (FSM) for the controller, by replacing data operations with setting and reading of control signals to and from the datapath.
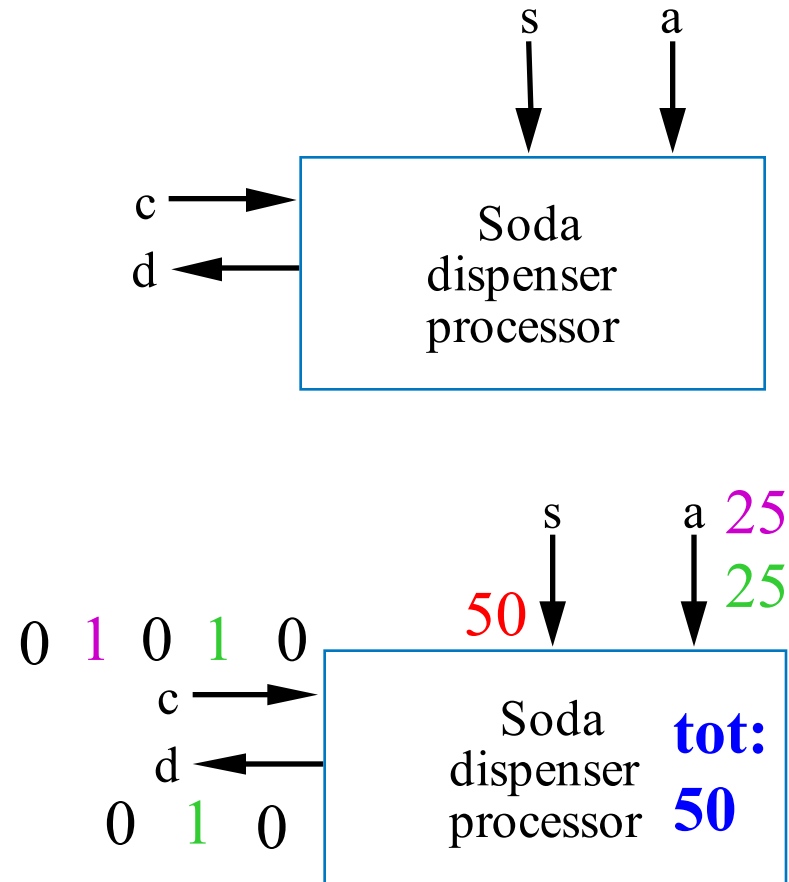
# Example: Vending Machine (Selling Soda)


- Soda dispenser
  - $c$ : 1-bit input, 1 when coin deposited
  - $a$ : 8-bit input having value of deposited coin
  - $s$ : 8-bit input having cost of a soda
  - $d$ : 1-bit output, processor sets to 1 when total value of deposited coins equals or exceeds cost of a soda



How can we precisely describe this processor's behavior?
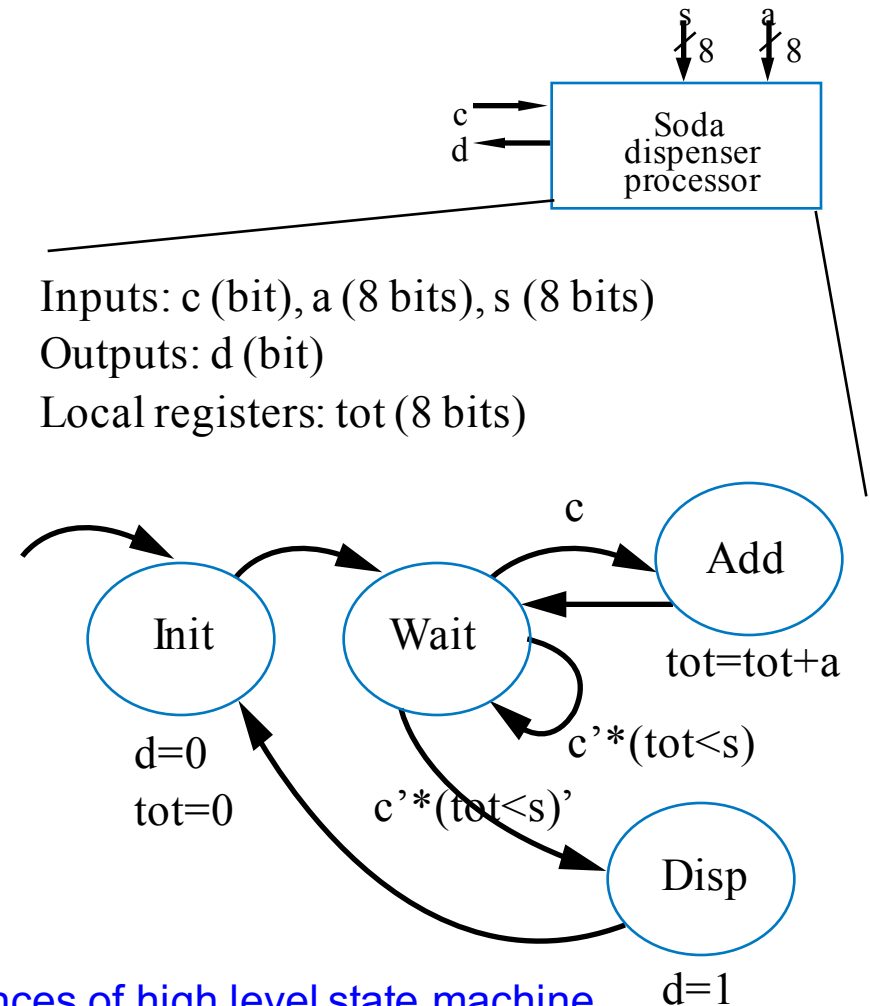
# Example: Step 1 – Capture High-Level State Machine

- Declare local register *tot*
- **Init** state: Set  $d=0$ ,  $tot=0$
- **Wait** state: wait for coin
  - If see coin, go to **Add** state
- **Add** state: Update total value:  
 $tot = tot + a$ 
  - Remember, *a* is present coin's value
  - Go back to **Wait** state
- In **Wait** state, if  $tot \geq s$ , go to **Disp** state
- **Disp** state: Set  $d=1$  (dispense soda)
  - Return to **Init** state



Differences of high level state machine

- Data types beyond just bits
- Arithmetic operations in states



# Example: Step 2 – Create Datapath

Inputs : c (bit), a(8 bits), s (8 bits)

Outputs : d (bit)


Local registers : tot (8 bits)

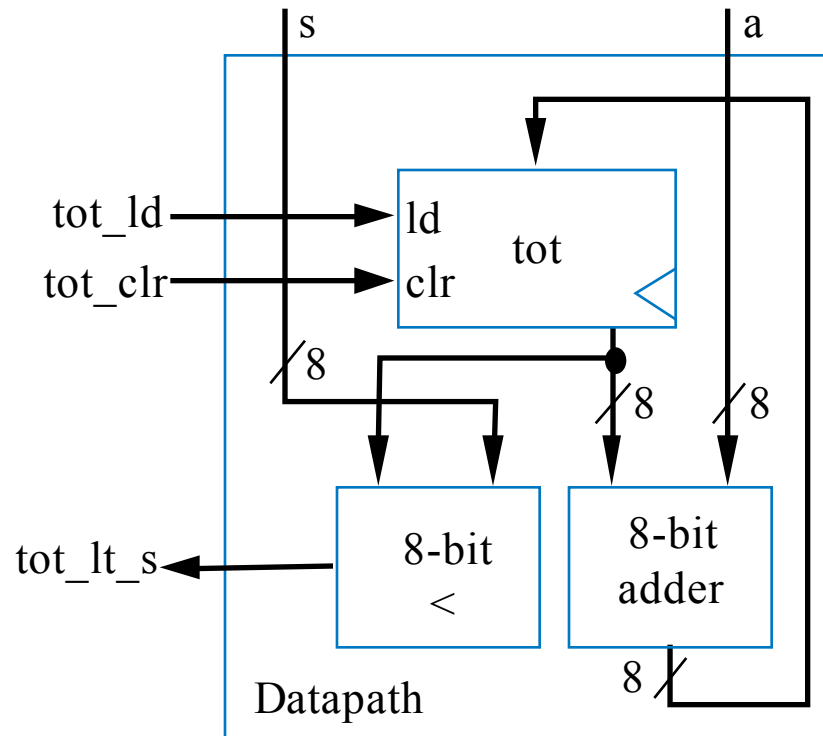 - Need *tot* register
  - To hold value between states
- Need 8-bit comparator
  - To compare s and *tot*
- Need 8-bit adder
  - To perform  $tot = tot + a$
- Create control input/outputs for datapath components
  - Give them names




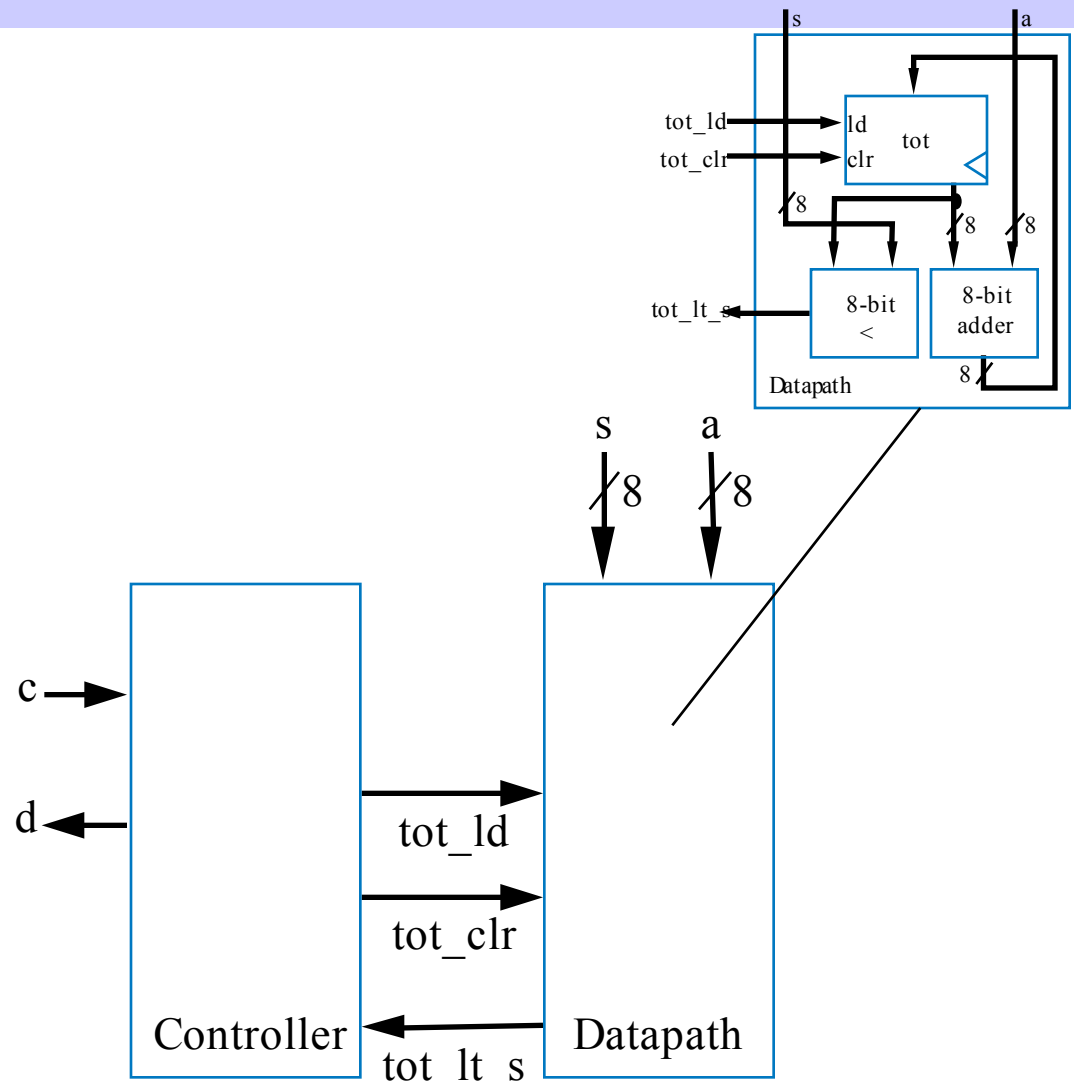
# Example: Step 3 – Connect Datapath to a Controller

- Identify controller's inputs
  - $c$  (coin detected)
  - comparator's output, which we named  $tot\_lt\_s$
- Identify controller's outputs
  - $d$  (dispense soda)
  - Signals to control datapath:  $tot\_ld$  and  $tot\_clr$


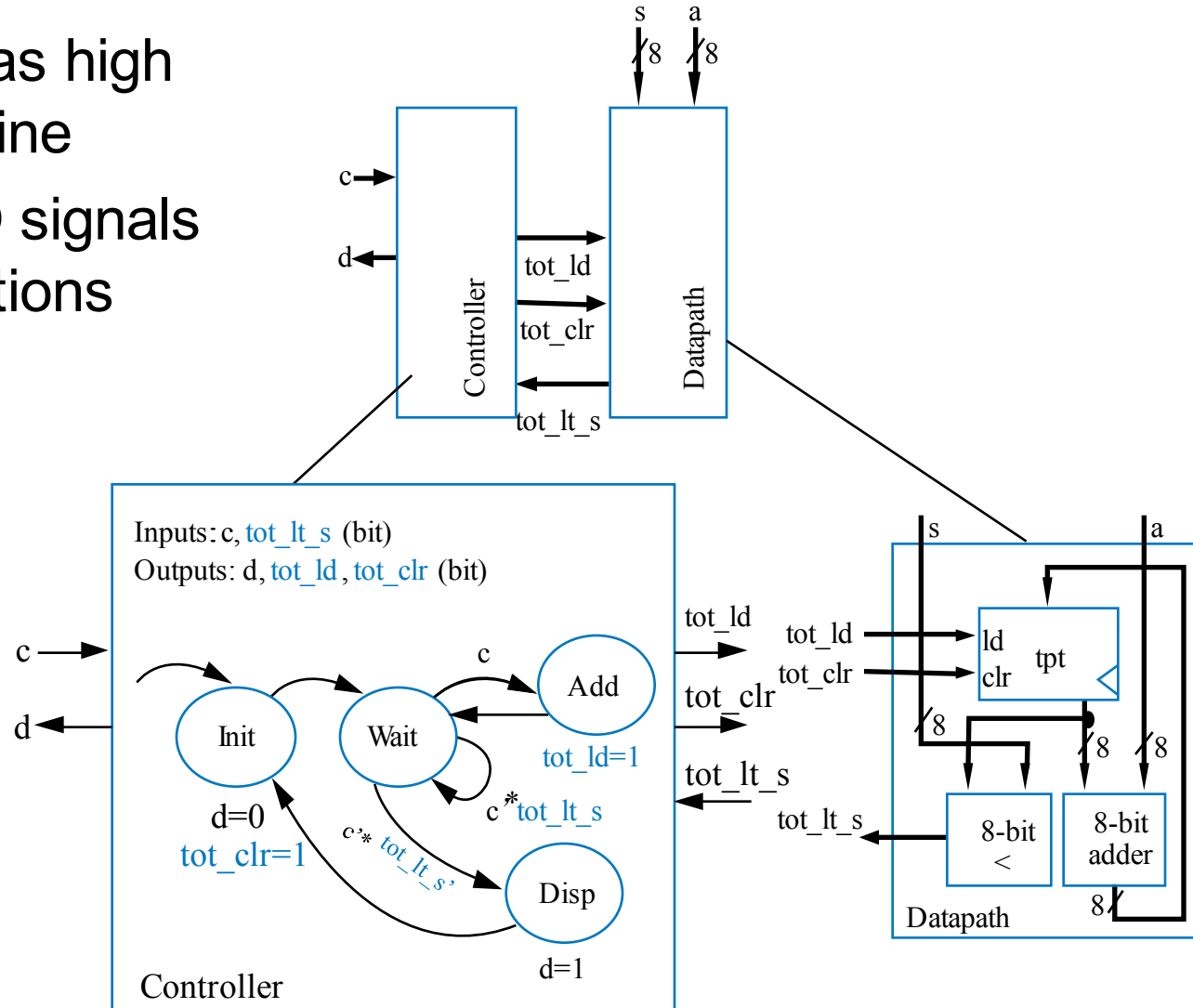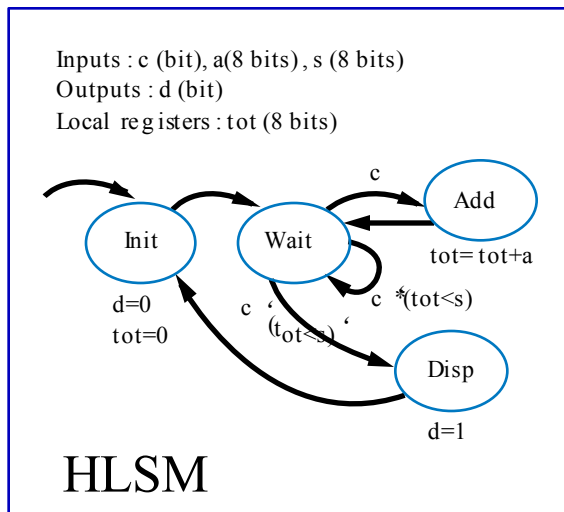
# Example: Step 4 – Derive the Controller's FSM


- Same structure as high level state machine
- But deal with I/O signals instead of operations





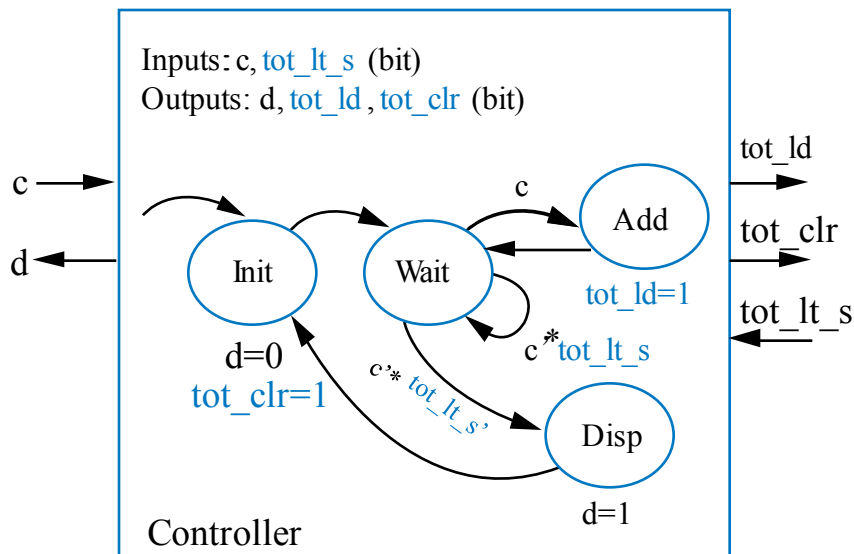
# Example: Completing the Design

- Implement the FSM as a state register and logic




	s1	s0	c	tot_lt_s	n1	n0	d	tot_ld	tot_clr
Init	0	0	0	0	0	1	0	0	1
	0	0	0	1	0	1	0	0	1
	0	0	1	0	0	1	0	0	1
	0	0	1	1	0	1	0	0	1
Wait	0	1	0	0	1	1	0	0	0
	0	1	0	1	0	1	0	0	0
	0	1	1	0	1	0	0	0	0
	0	1	1	1	1	0	0	0	0
Add	1	0	0	0	0	1	0	1	0
			...			...			
Disp	1	1	0	0	0	0	1	0	0
			...			...			

# Example: Laser-Based Distance Measurer

 

- Laser-based distance measurement – pulse laser, measure time  $T$  to sense reflection
  - Laser light travels at speed of light,  $3 * 10^8 \text{ m/sec}$
  - Distance is thus  $D = T \text{ sec} * 3 * 10^8 \text{ m/sec} / 2$

# Example: Laser-Based Distance Measurer

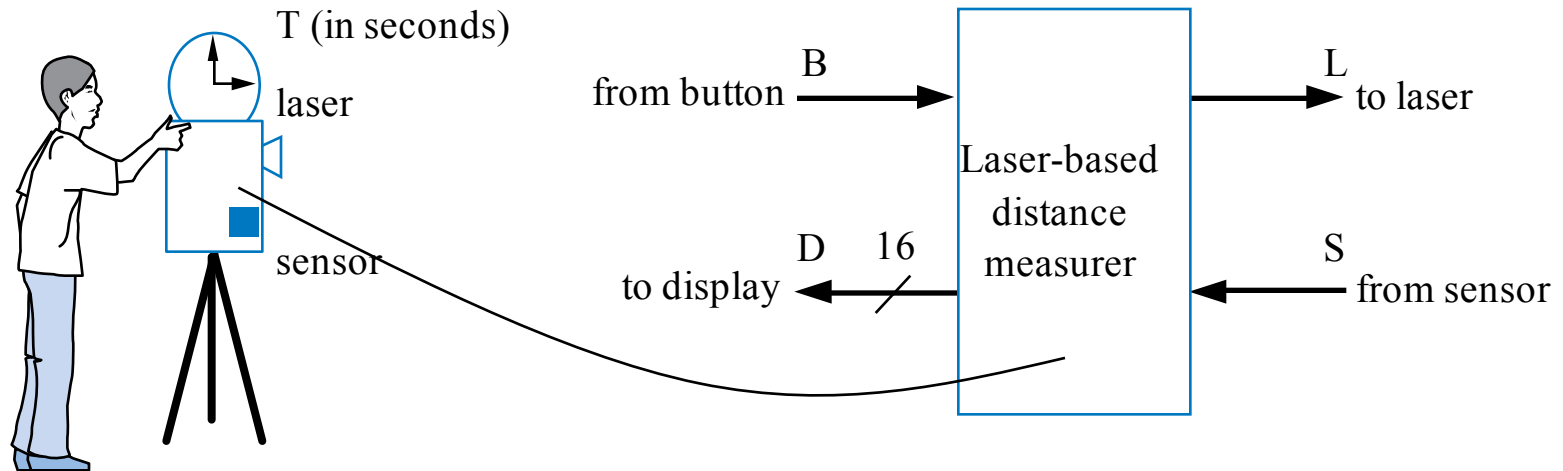


- Inputs/outputs
  - *B*: 1-bit input, from button to begin measurement
  - *L*: 1-bit output, activates laser
  - *S*: 1-bit input, senses laser reflection
  - *D*: 16-bit output, displays computed distance

# Step 1: Capture High-Level State Machine


Inputs: B, S (1 bit each)

Outputs: L (bit), D (16 bits)

 

L = 0 (laser off)



D = 0 (distance = 0)

 

- Step 1: Create high-level state machine
  - Begin by declaring inputs and outputs
  - Create initial state, name it **S0**
    - Initialize laser to off (L=0)
    - Initialize displayed distance to 0 (D=0)
  
# Step 1: Capture High-Level State Machine

Inputs: B, S (1 bit each)  
Outputs: L (bit), D (16 bits)





- Add another state, call **S1**, that waits for a button press
  - **B'** – stay in **S1**, keep waiting
  - **B** – go to a new state **S2**

**Q: What should S2 do?**    **A: Turn on the laser**
  
# Step 1: Capture High-Level State Machine

Inputs: B, S (1 bit each)  
Outputs: L (bit), D (16 bits)





- Add a state **S2** that turns on the laser (L=1)
- Then turn off laser (L=0) in a state **S3**

**Q: What do next?** A: Start timer, wait to sense reflection

# Step 1: Capture High-Level State Machine

Inputs: B, S (1 bit each)      Outputs: L (bit), D (16 bits)

Local Registers: Dctr (16 bits)

 
 


- Stay in **S3** until sense reflection (S)
- To measure time, count cycles for which we are in **S3**
  - To count, declare local register  $Dctr$
  - Increment  $Dctr$  each cycle in **S3**
  - Initialize  $Dctr$  to 0 in **S1**. **S2** would have been O.K. too

**Q: What do next?**    A: Stop timer, calculate distance
  
# Step 1: Capture High-Level State Machine

Inputs: B, S (1 bit each)    Outputs: L (bit), D (16 bits)  
Local Registers: Dctr (16 bits)




- Once reflection detected (S), go to new state **S4**
  - Calculate distance
  - Assuming clock frequency is  $3 \times 10^8$ ,  $Dctr$  holds number of meters, so  $D = Dctr / 2$
- After **S4**, go back to **S1** to wait for button again



## Step 2: Create a Datapath


- Datapath must
  - Implement data storage
  - Implement data computations
- Look at high-level state machine, instantiate required components

## Step 2: Create a Datapath

 

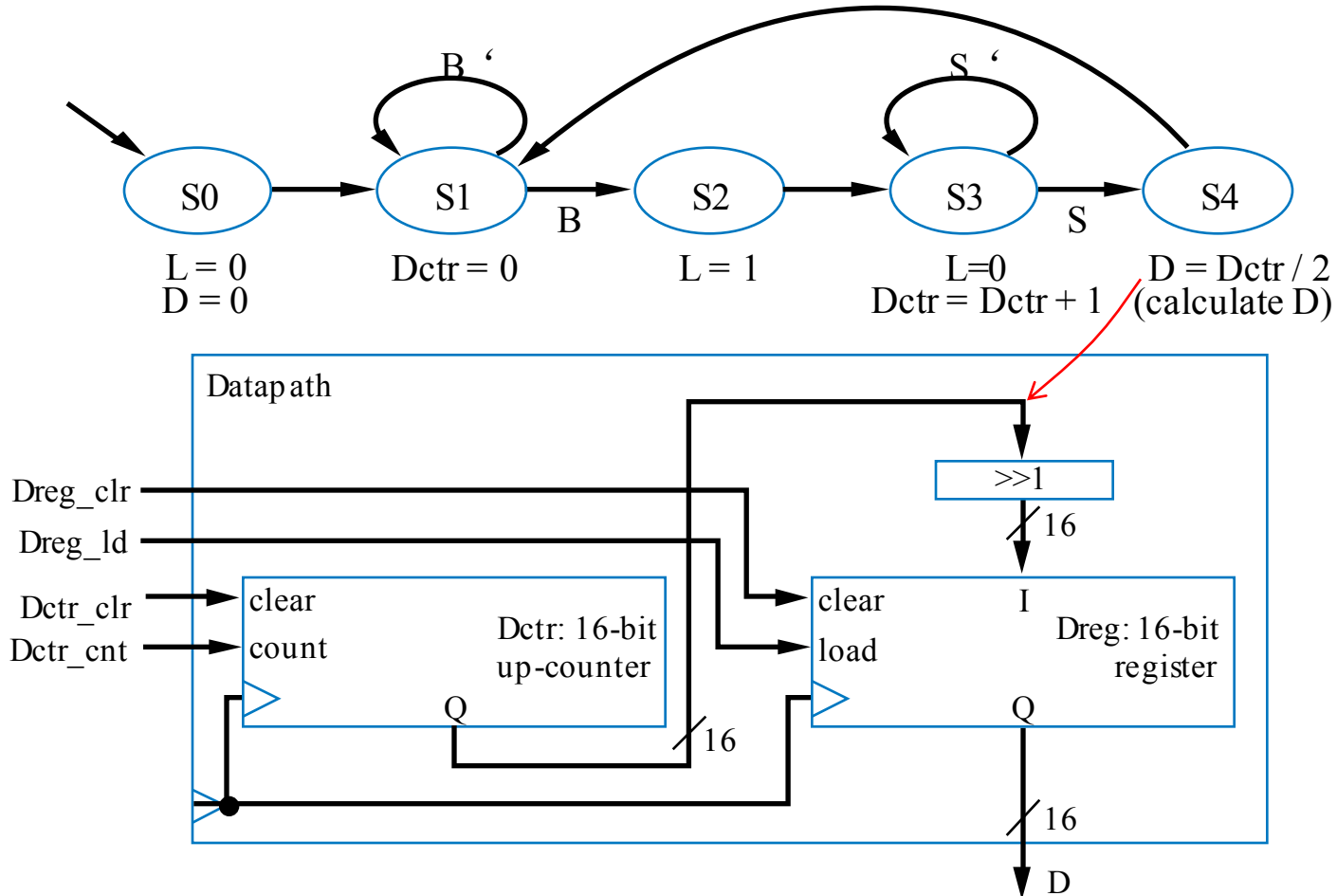
# Step 2: Create a Datapath


Inputs: B, S (1 bit each)      Outputs: L (bit), D (16 bits)  
Local Registers: Dctr (16 bits)



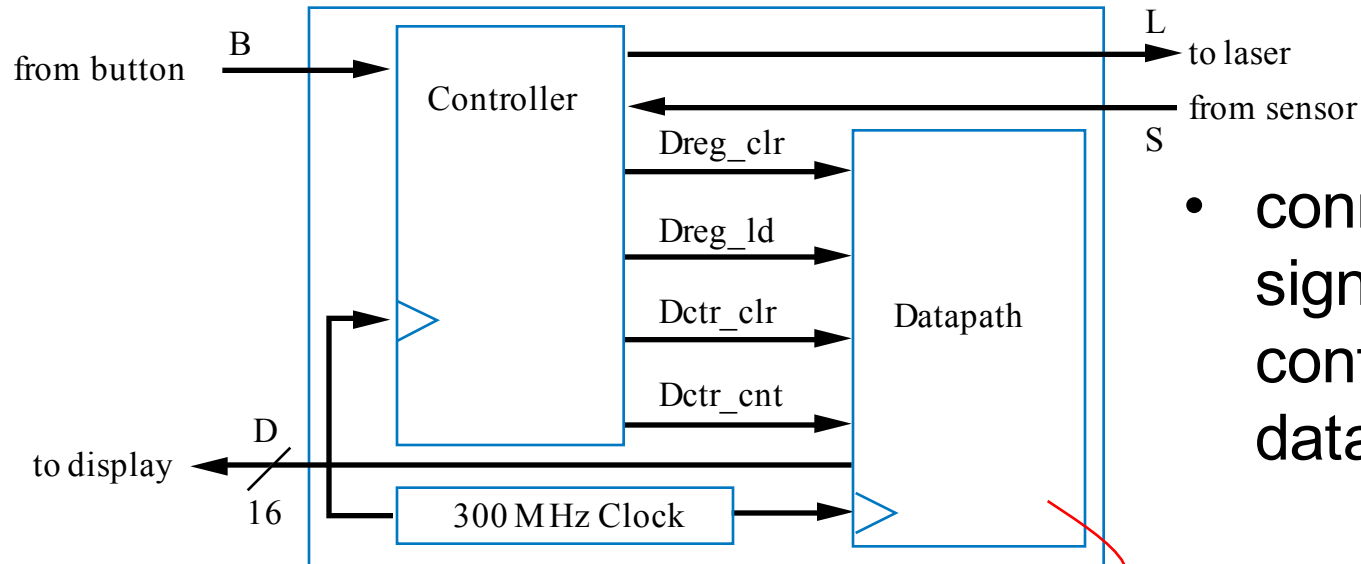
# Step 3: Connecting the Datapath to a Controller



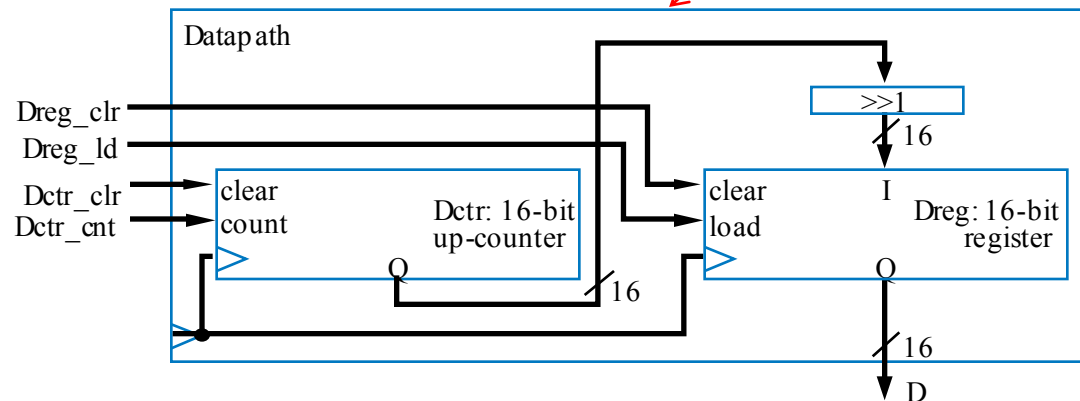
- connect all control signals between controller and datapath



# Step 4: Deriving the Controller's FSM

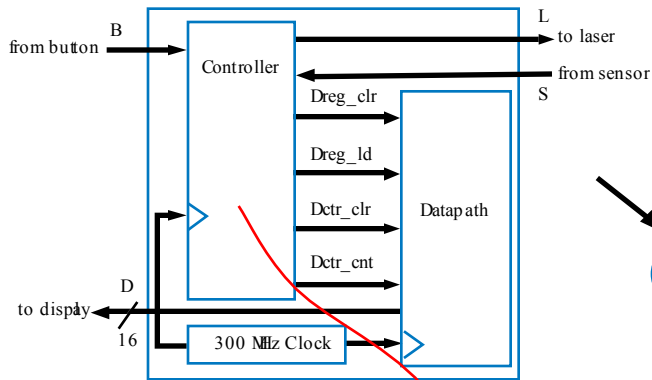


 Inputs: B, S (1 bit each)      Outputs: L (bit), D (16 bits)  
Local Registers: Dctr (16 bits)




- Replace data operations by bit operations using datapath

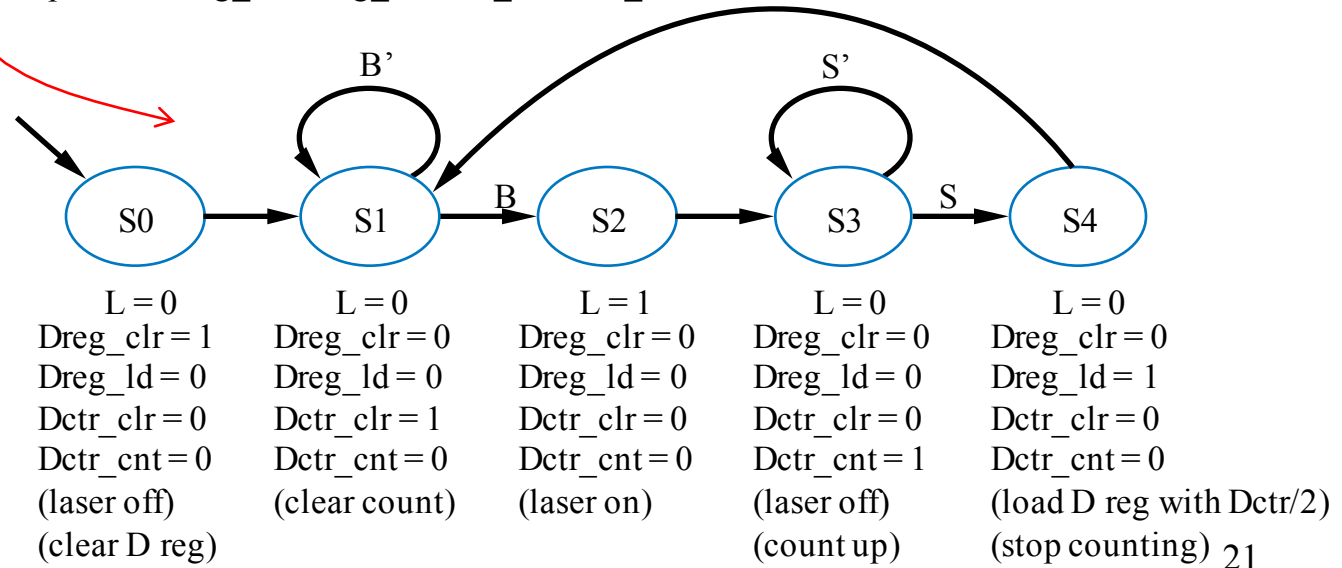
Inputs: B, S  
Outputs: L, Dreg\_clr, Dreg\_ld, Dctr\_clr, Dctr\_cnt




# Step 4: Deriving the Controller's FSM

 

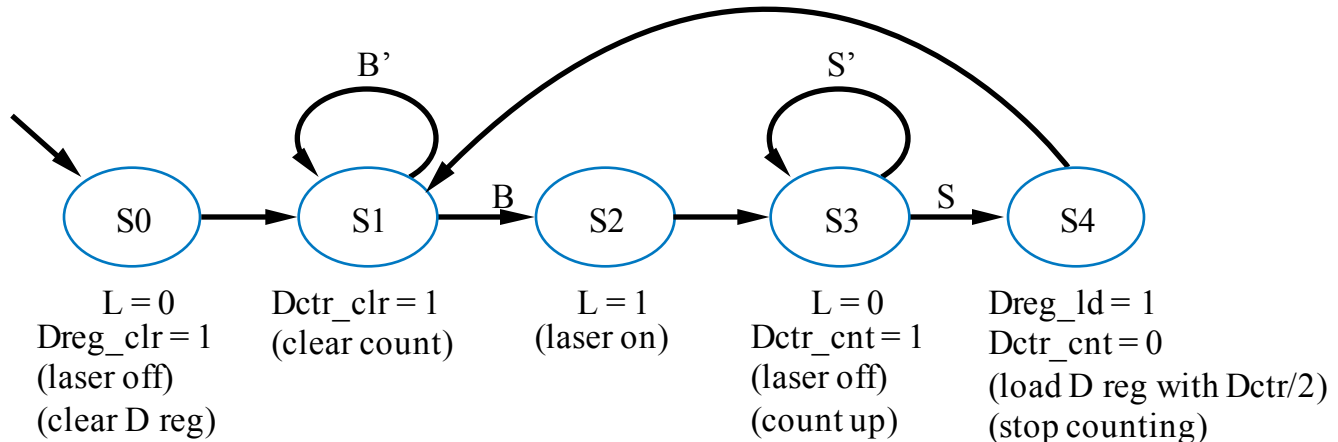
Inputs: B, S    Outputs: L, Dreg\_clr, Dreg\_ld, Dctr\_clr, Dctr\_cnt



# Step 4: Deriving the Controller's FSM

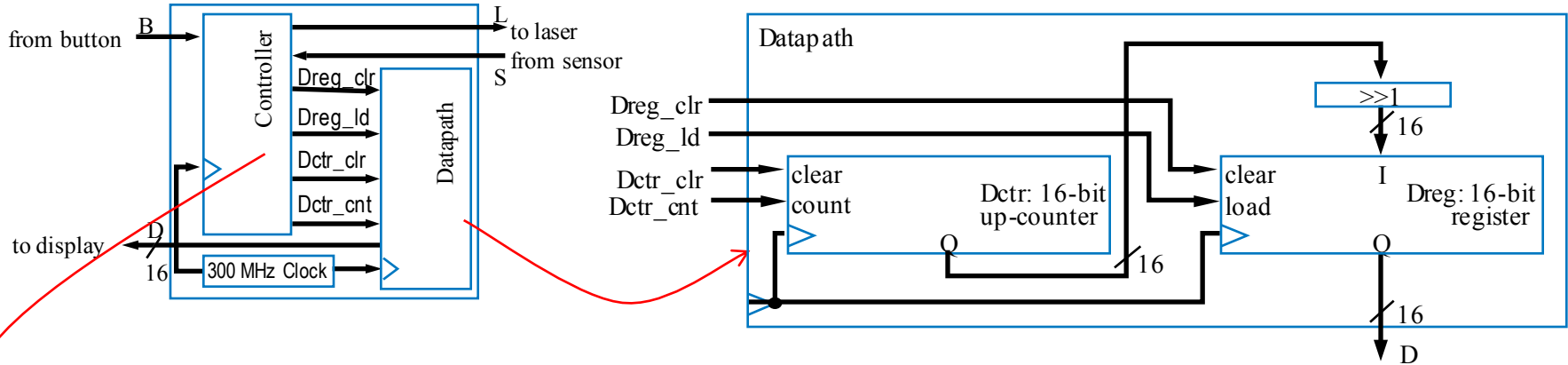


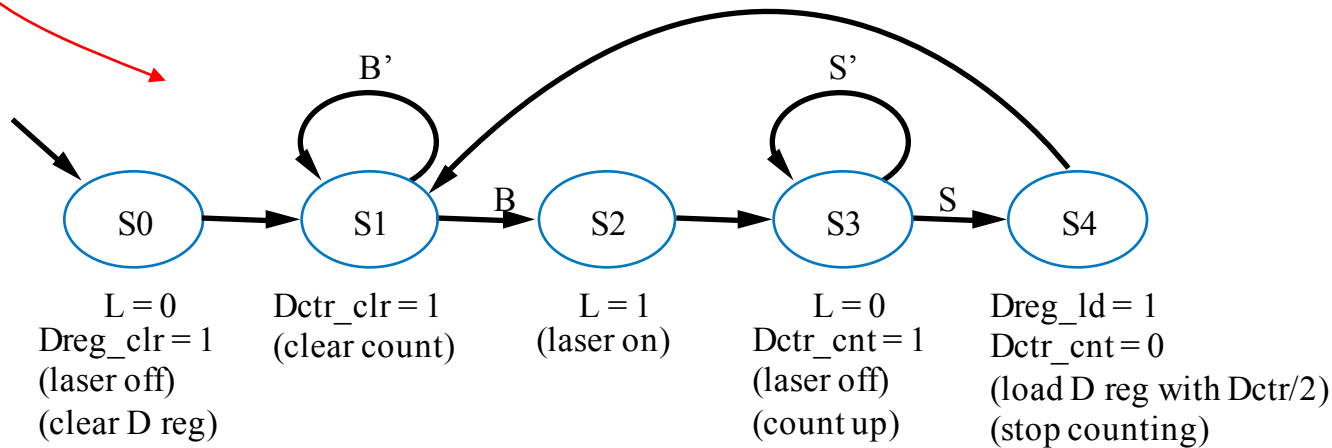Inputs: B, S    Outputs: L, Dreg\_clr, Dreg\_ld, Dctr\_clr, Dctr\_cnt




# RTL Example: Bus Interface

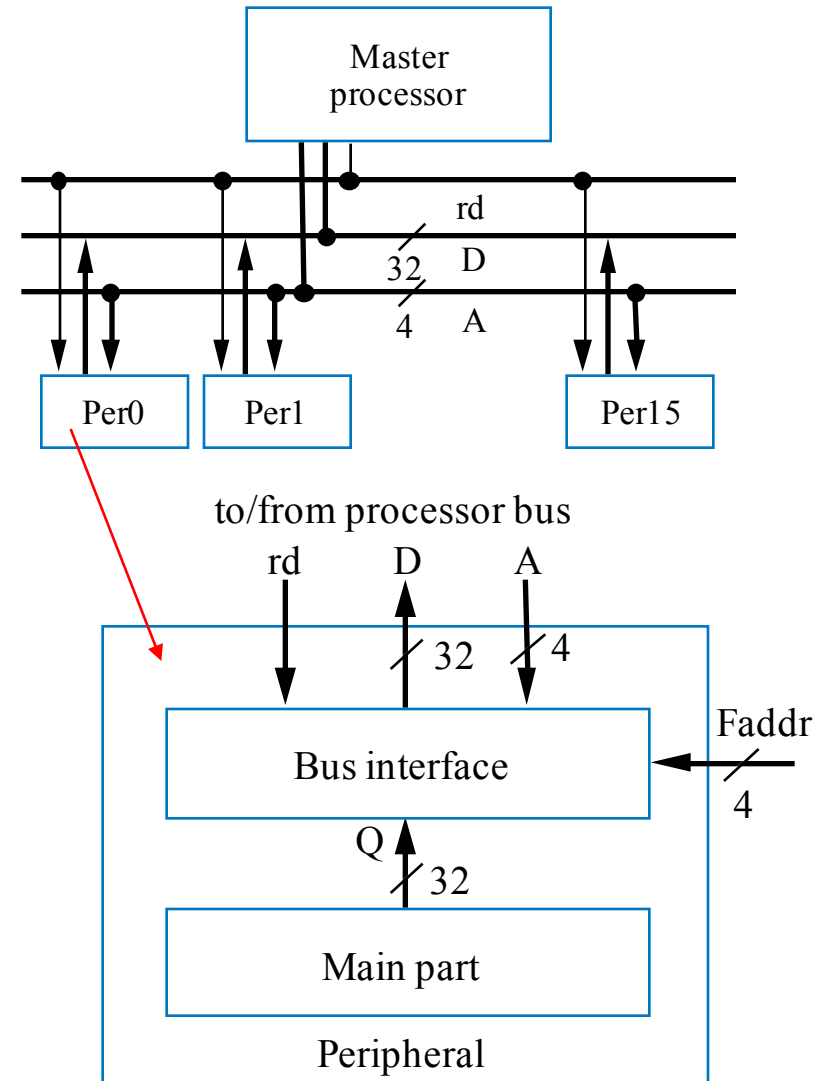- Example: **Bus interface**
  - Master processor can read register from any peripheral
    - Each register has unique 4-bit address
    - Assume 1 register/peripheral
  - Sets  $rd=1$ ,  $A=address$
  - Appropriate peripheral places register data on 32-bit  $D$  lines
    - Peripheral's address provided on  $Faddr$  inputs (maybe from DIP switches, or another register)






# RTL Example: Bus Interface

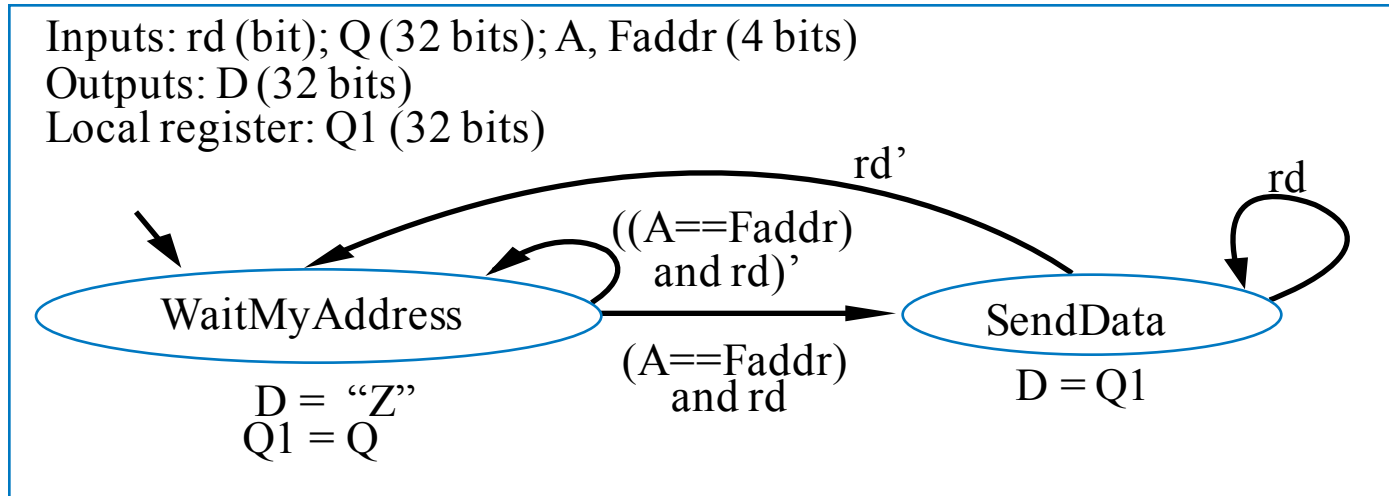


- Step 1: Create high-level state machine
  - State **WaitMyAddress**
    - Output “nothing” (“Z”) on  $D$ , store peripheral’s register value  $Q$  into local register  $Q1$
    - Wait until this peripheral’s address is seen ( $A == Faddr$ ) and  $rd = 1$
  - State **SendData**
    - Output  $Q1$  onto  $D$ , wait for  $rd = 0$  (meaning main processor is done reading the  $D$  lines)

# RTL Example: Bus Interface

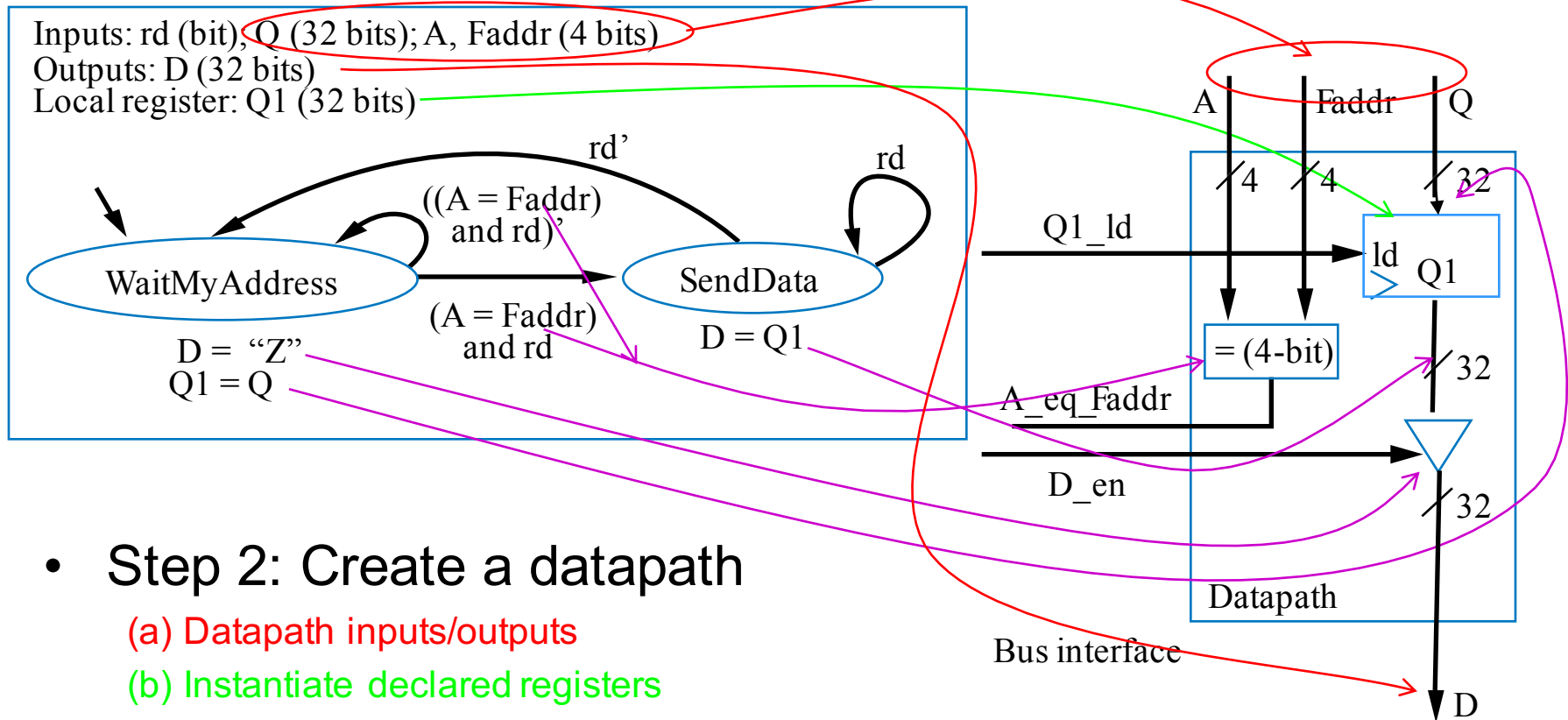

- Step 2: Create a datapath
  - (a) Datapath inputs/outputs
  - (b) Instantiate declared registers
  - (c) Instantiate datapath components and connections

# RTL Example: Bus Interface

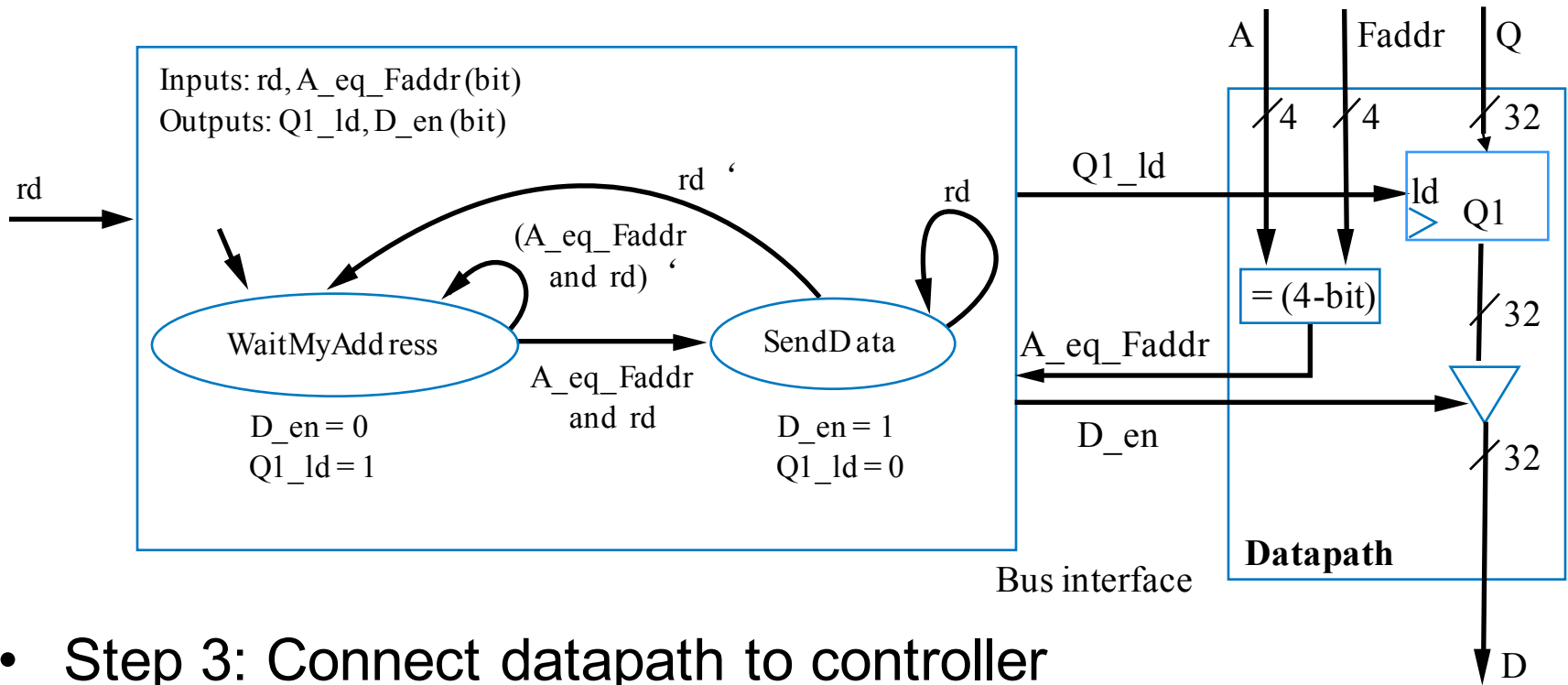


- Step 3: Connect datapath to controller
- Step 4: Derive controller's FSM

# Handle the Complexity with Hierarchical Design


- Hierarchical design structure at different levels of abstraction
- Levels of abstraction: hiding the details in lower levels

- Hide details
- Reuse subsystems

 


Hierarchical Structure of a Design



# Hierarchical Digital System

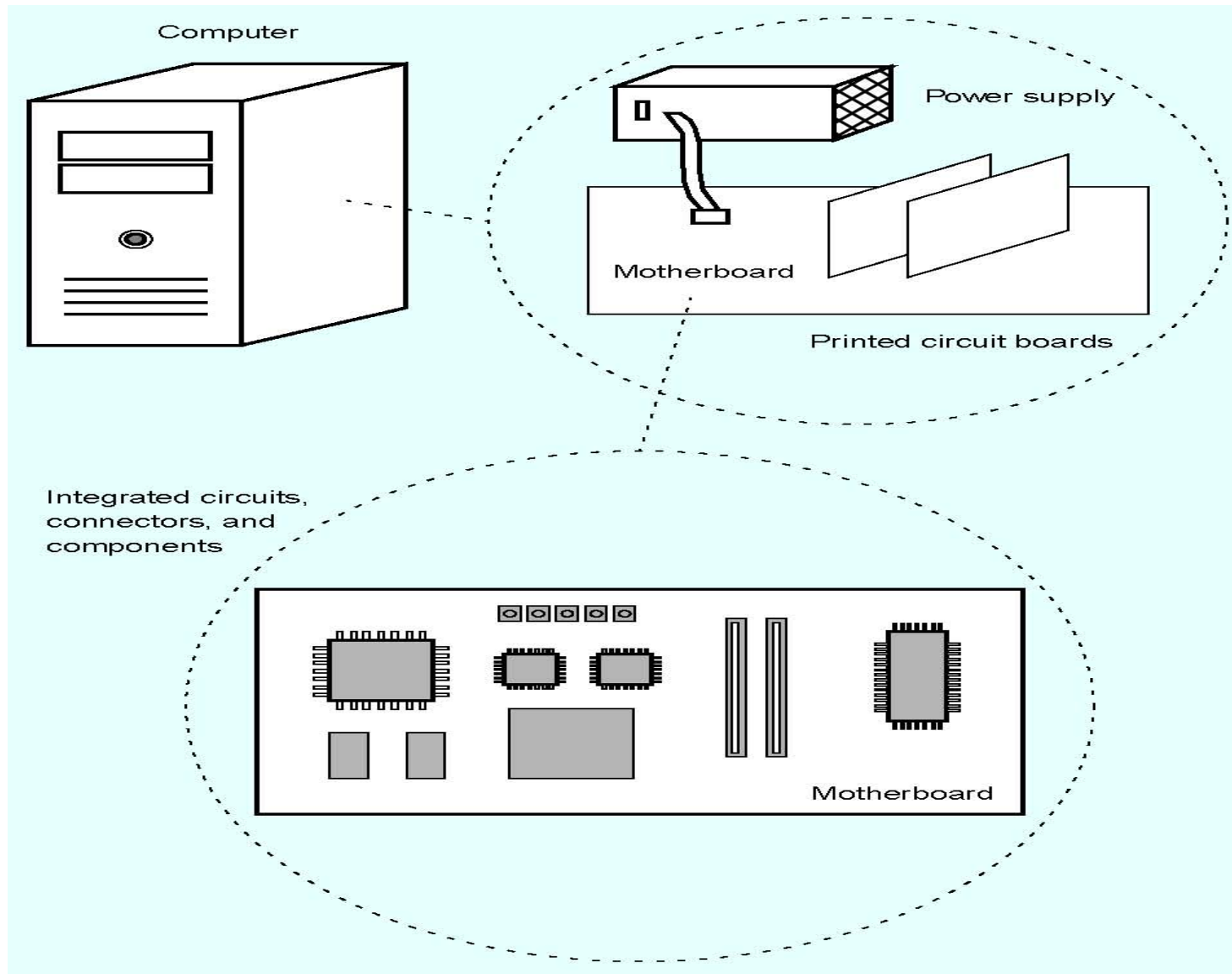



# Hierarchical Digital System

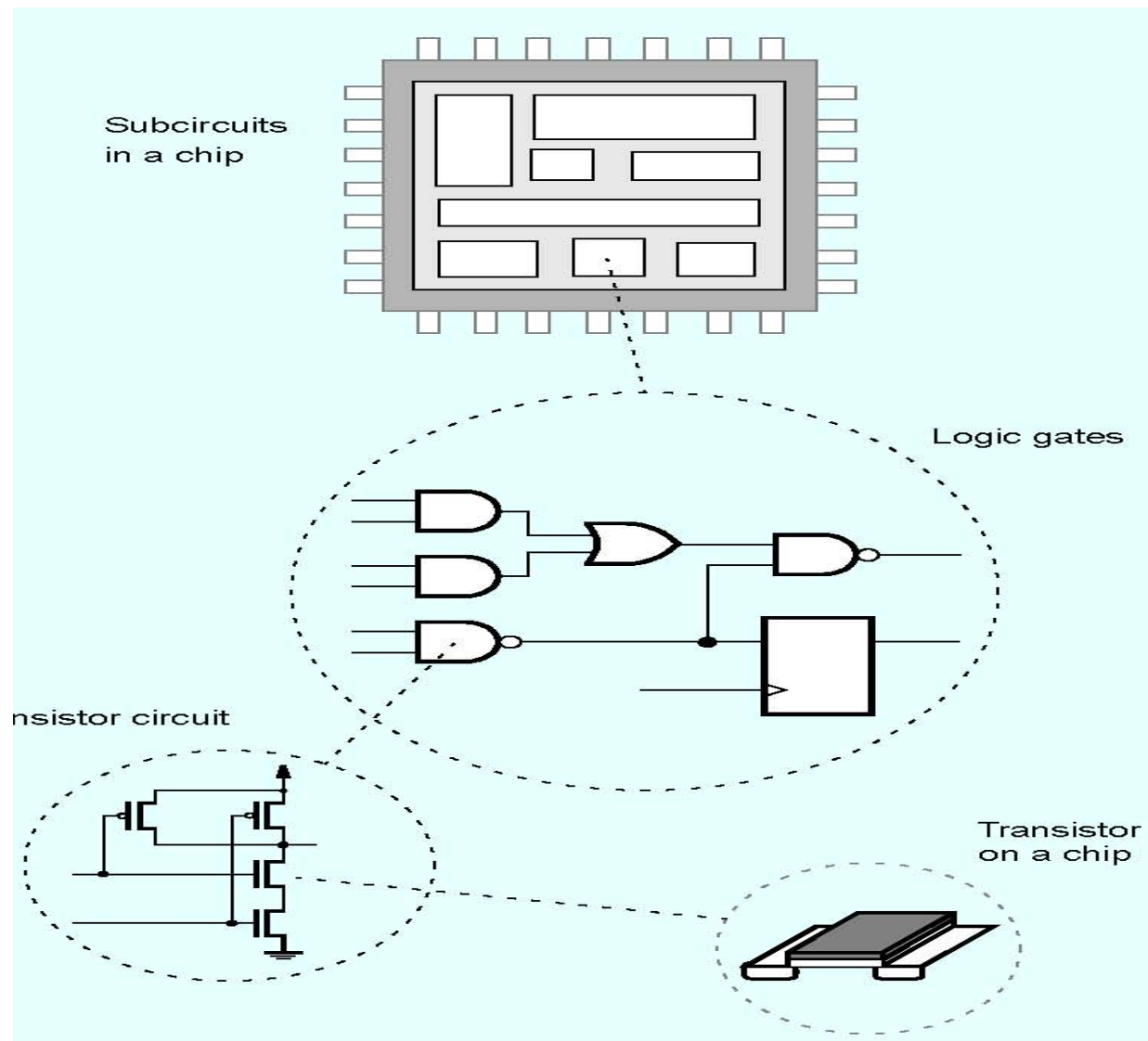



# Pacemaker

  


**Figure 3.68** Pacemaker with leads (left), and pacemaker's location under the skin (right). Courtesy of Medtronic, Inc.

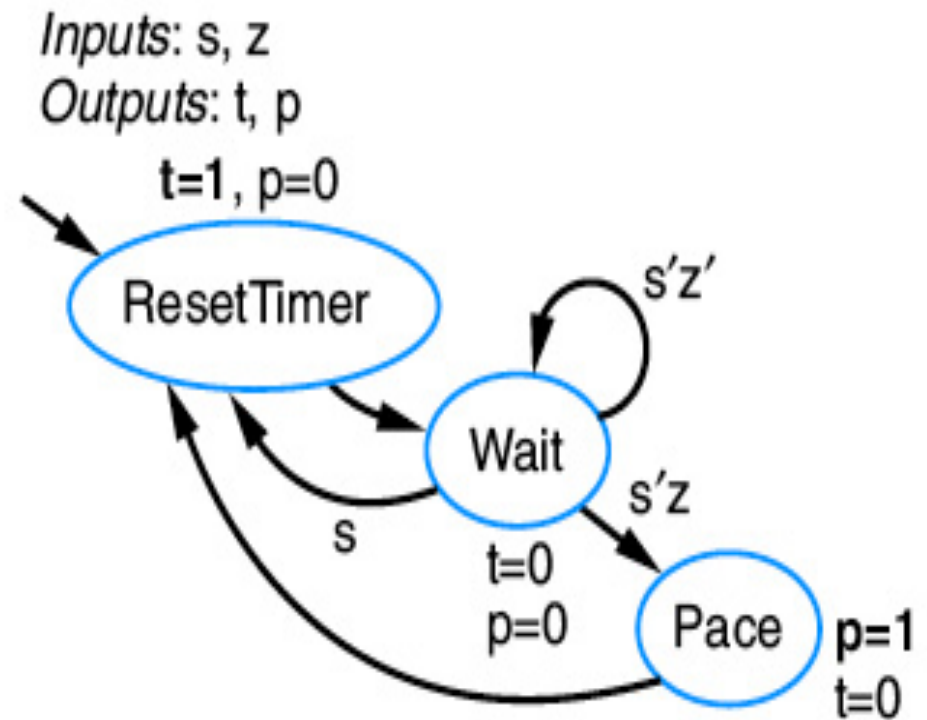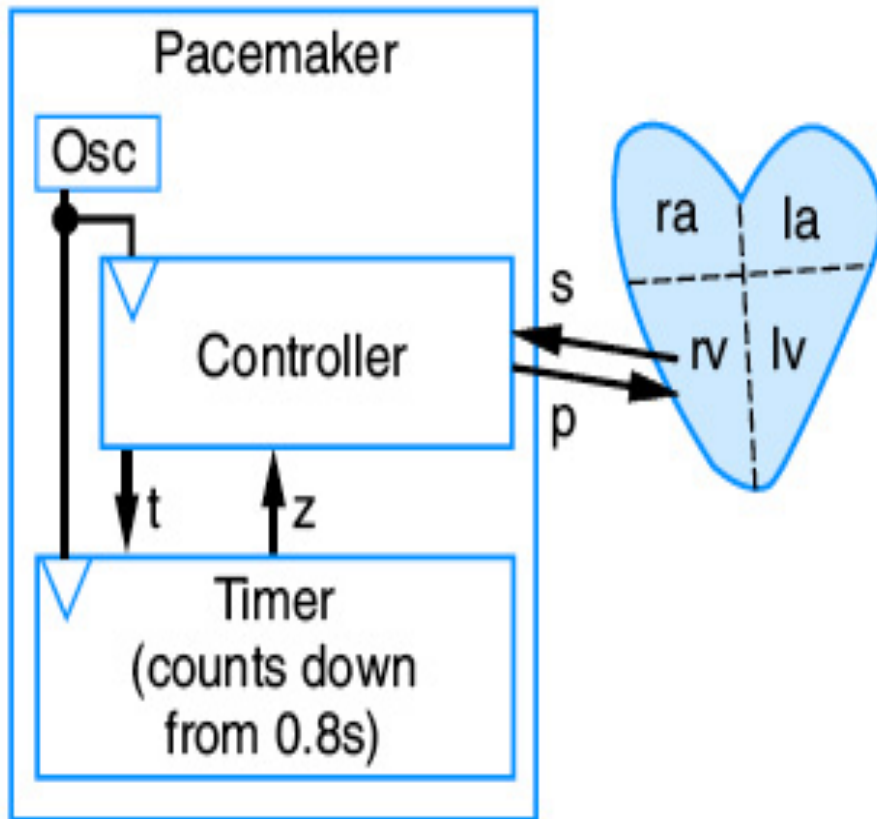




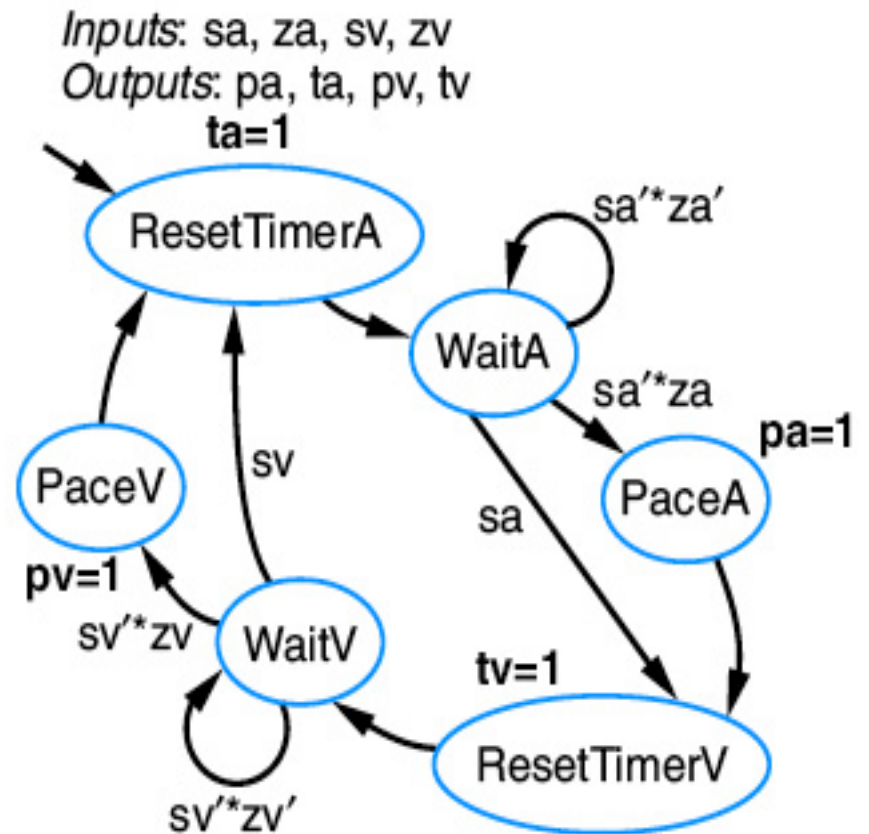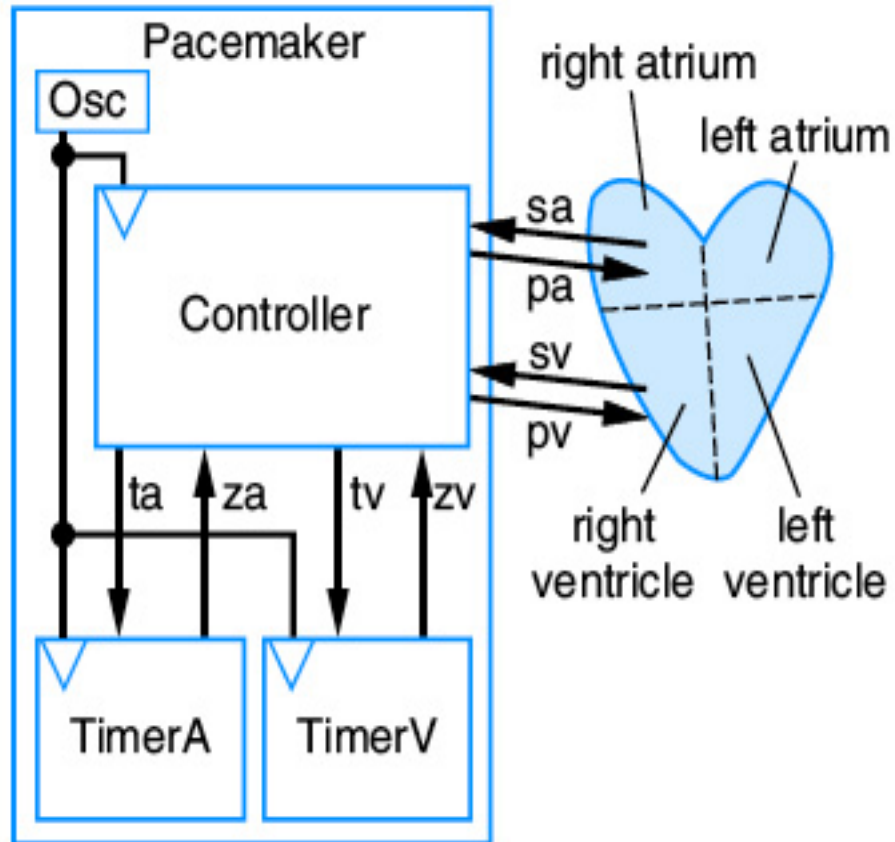

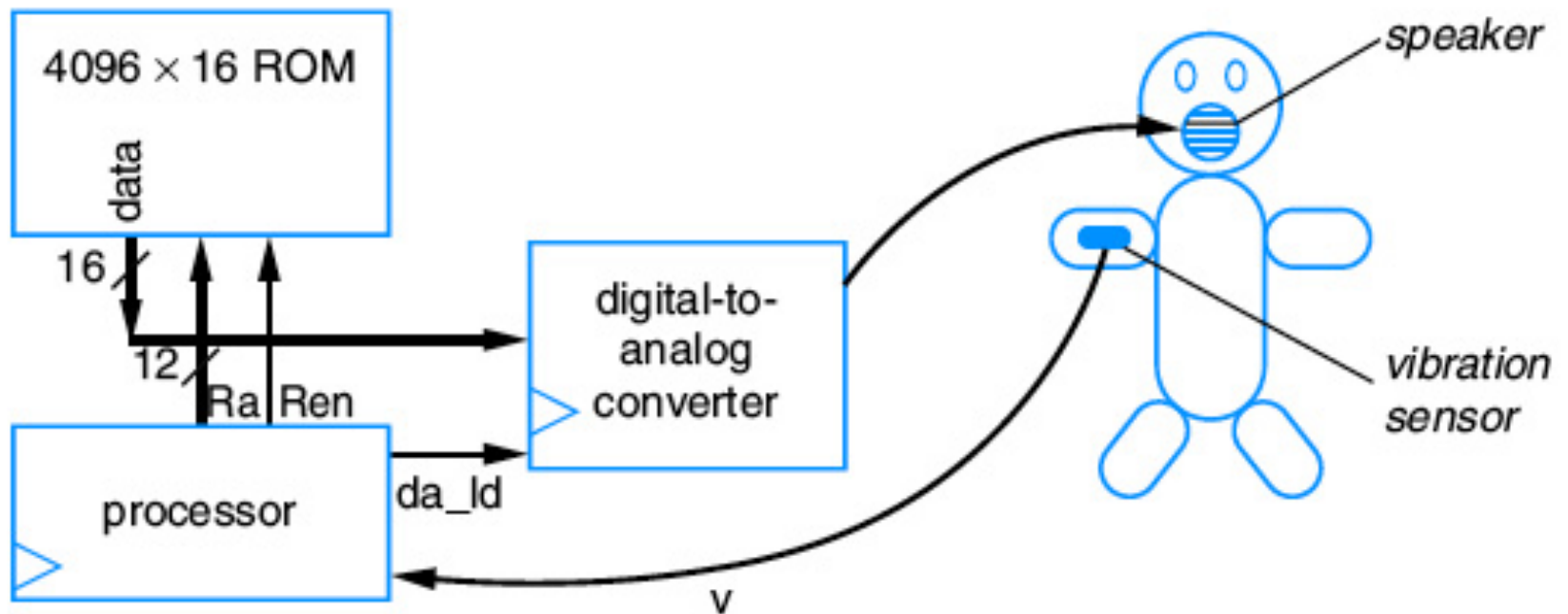
# Talking Doll




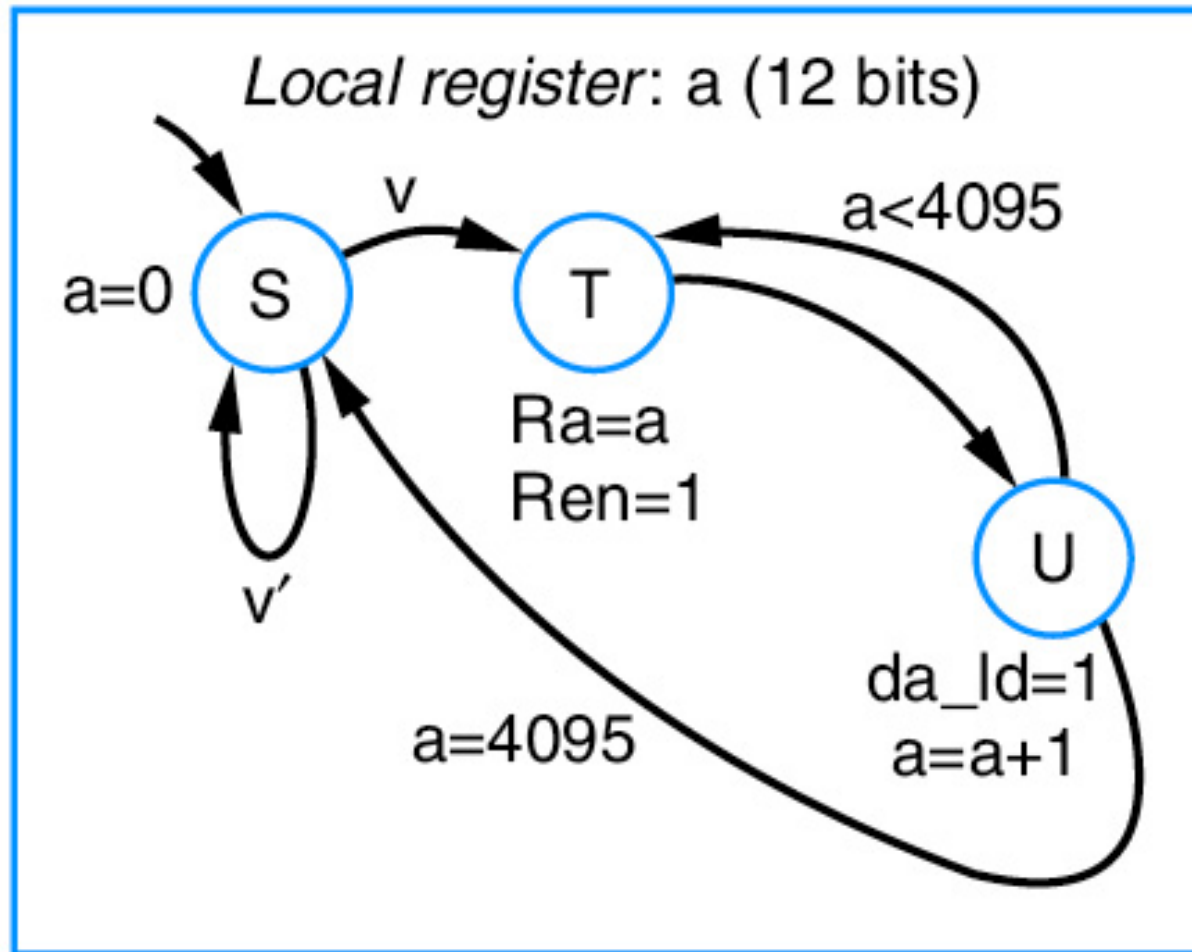


**Figure 5.72** State machine for reading the ROM.
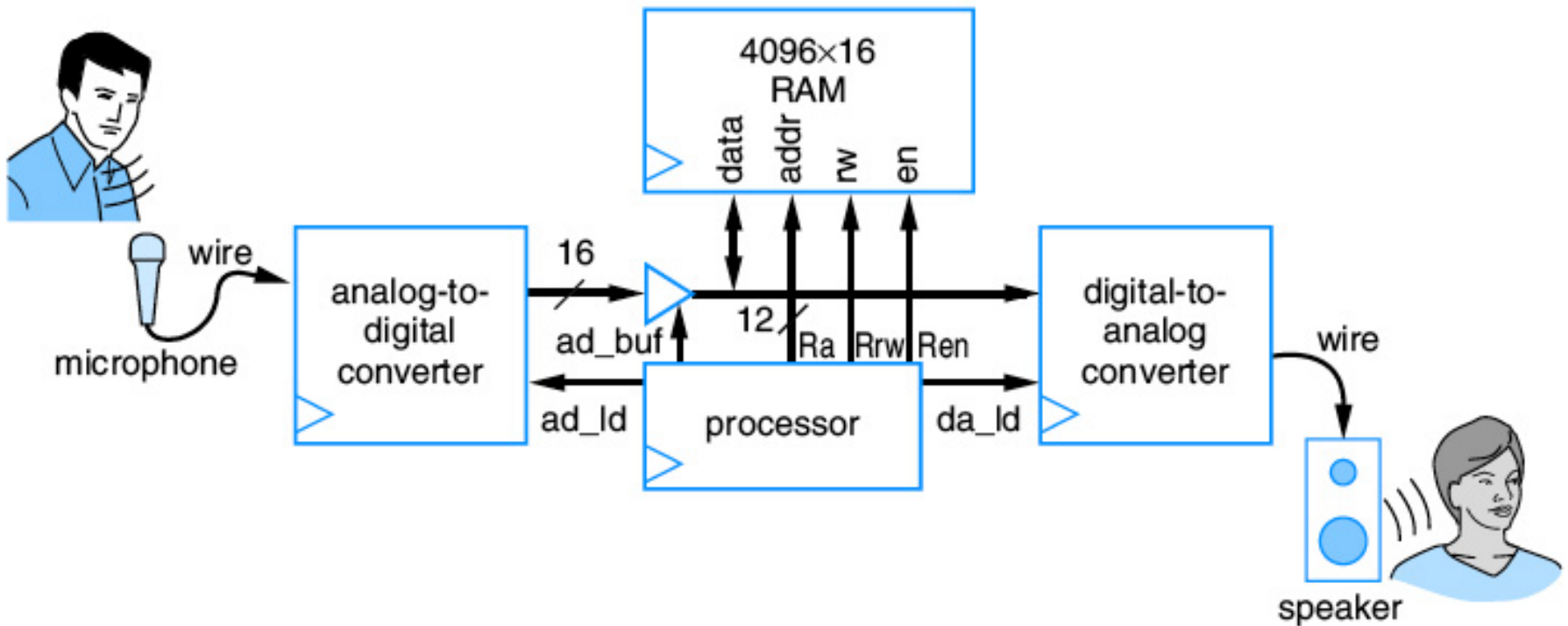
# Answering Machine



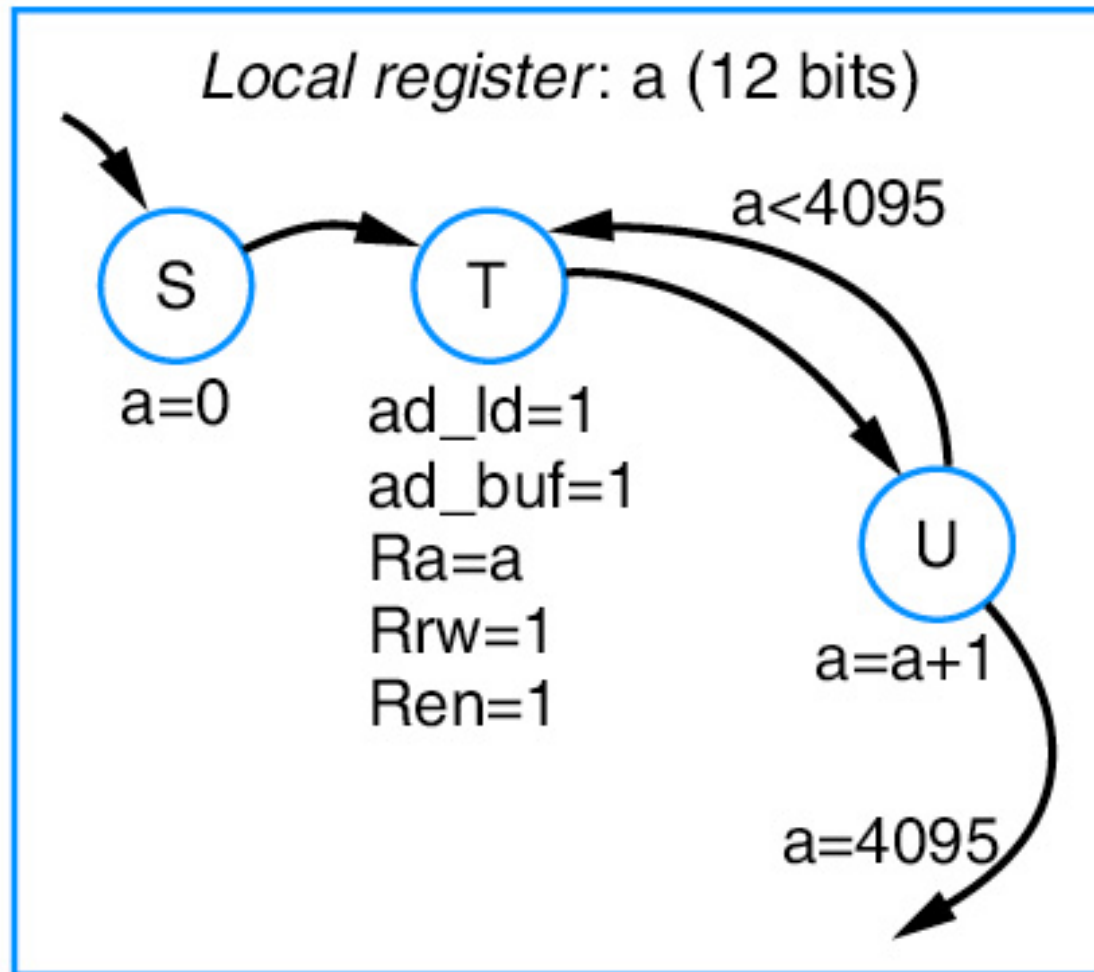

**Figure 5.62** State machine for storing digitized sound in RAM.

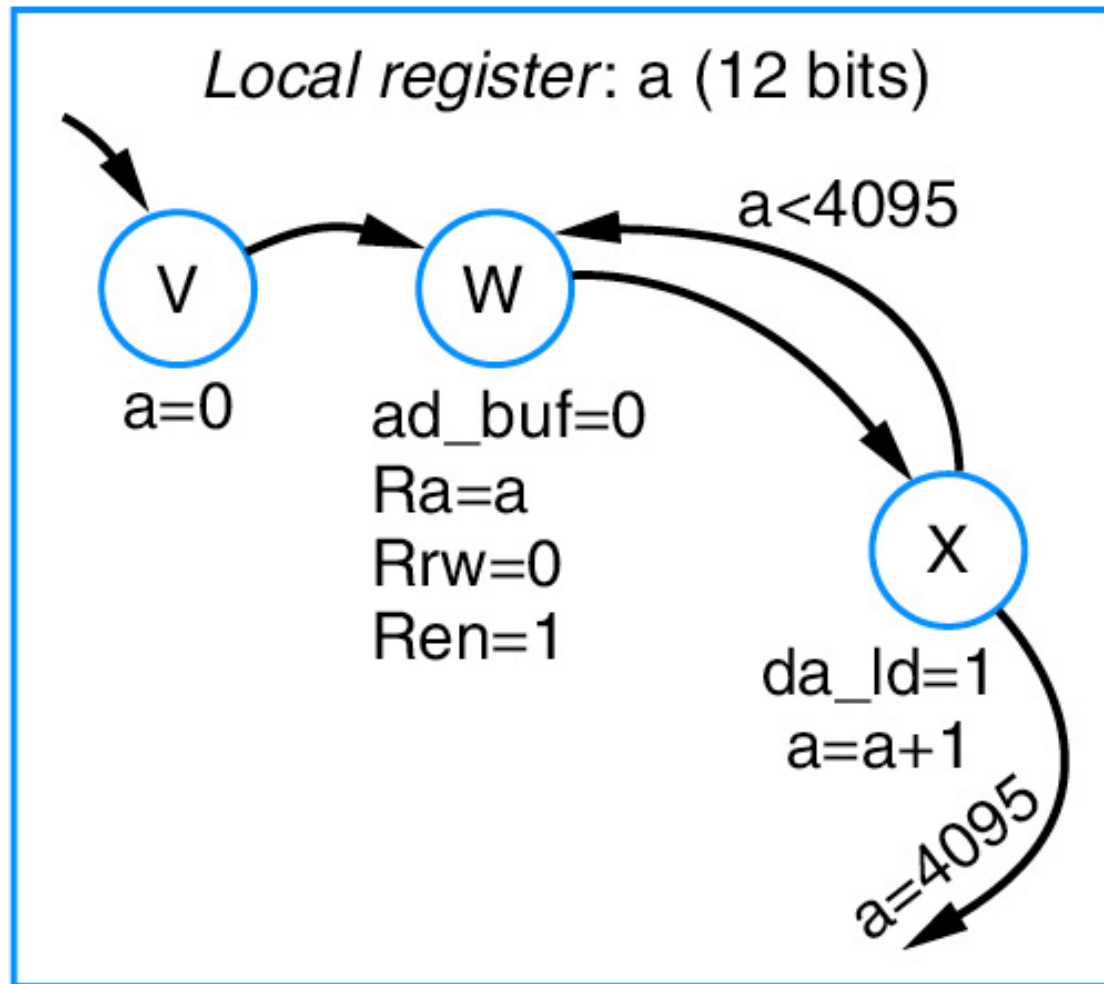

**Figure 5.63** State machine for playing sound from the RAM.