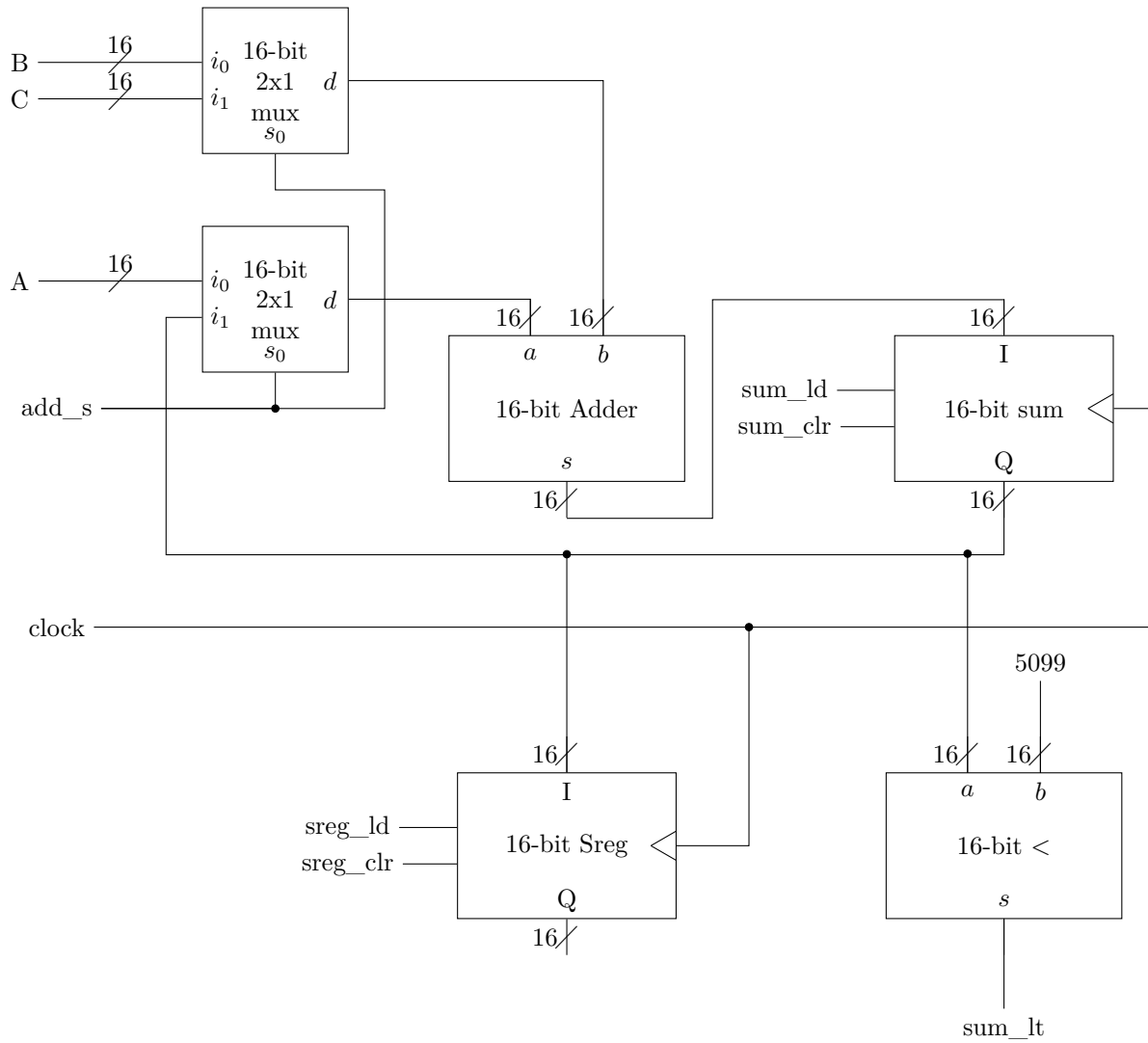


VE270 Homework 9

Liu Yihao 515370910207

Problem 1.

Inputs: A, B, C, add_s (0 for sum:=A+B and 1 for sum:=sum+C), sum_ld, sum_clr, sreg_ld, sreg_clr, clock
 Outputs: sum_lt (whether sum<5099)



Problem 2.

