

# VE270 Homework 10

Liu Yihao 515370910207

## Problem 1.

(a) The truth table is

$s_2$	$s_1$	$s_0$	$B$	$S$	$n_2$	$n_1$	$n_0$	$L$	$Dreg\_clr$	$Dreg\_ld$	$Dctr\_clr$	$Dctr\_ld$
0	0	0	0	0	0	0	1	0	1	0	0	0
0	0	0	0	1	0	0	1	0	1	0	0	0
0	0	0	1	0	0	0	1	0	1	0	0	0
0	0	0	1	1	0	0	1	0	1	0	0	0
0	0	1	0	0	0	0	1	0	0	0	1	0
0	0	1	0	1	0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0	0	0	0	1	0
0	0	1	1	1	0	1	0	0	0	0	1	0
0	1	0	0	0	0	1	1	1	0	0	0	0
0	1	0	0	1	0	1	1	1	0	0	0	0
0	1	0	1	0	0	1	1	1	0	0	0	0
0	1	0	1	1	0	1	1	1	0	0	0	0
0	1	1	0	0	0	1	1	0	0	0	0	1
0	1	1	0	1	1	0	0	0	0	0	0	1
0	1	1	1	0	0	1	1	0	0	0	0	1
0	1	1	1	1	1	0	0	0	0	0	0	1
1	0	0	0	0	0	0	1	0	0	1	0	0
1	0	0	0	1	0	0	1	0	0	1	0	0
1	0	0	1	0	0	0	1	0	0	1	0	0
1	0	0	1	1	0	0	1	0	0	1	0	0
1	0	1	0	0	X	X	X	X	X	X	X	X
1	0	1	0	1	X	X	X	X	X	X	X	X
1	0	1	1	0	X	X	X	X	X	X	X	X
1	0	1	1	1	X	X	X	X	X	X	X	X
1	1	0	0	0	X	X	X	X	X	X	X	X
1	1	0	0	1	X	X	X	X	X	X	X	X
1	1	0	1	0	X	X	X	X	X	X	X	X
1	1	0	1	1	X	X	X	X	X	X	X	X
1	1	1	0	0	X	X	X	X	X	X	X	X
1	1	1	0	1	X	X	X	X	X	X	X	X
1	1	1	1	0	X	X	X	X	X	X	X	X
1	1	1	1	1	X	X	X	X	X	X	X	X

The equations are

$$n_2 = s_1 s_0 S$$

$$n_1 = s'_1 s_0 B + s_1 s'_0 + s_1 S'$$

$$n_0 = s'_1 B' + s_1 S' + s'_0$$

$$L = s_1 s'_0$$


$$Dreg\_clr = s'_2 s'_1 s'_0$$

$$Dreg\_ld = s_2$$

$$Dctr\_clr = s'_1 s_0$$

$$Dctr\_ld = s_1 s_0$$

The schematics is

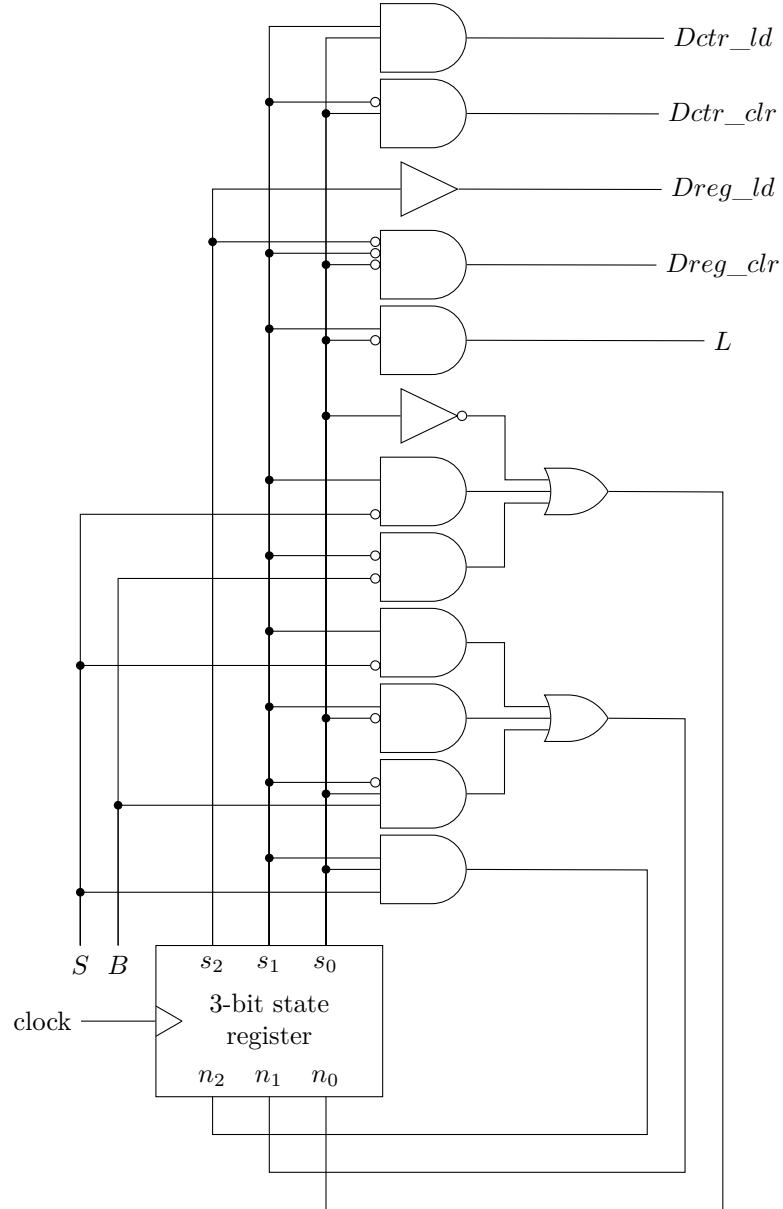

(b) The critical path is the 16-bit up counter, so the delay is 5 ns.

(c) The maximum clock frequency is  $1/5 \text{ ns} = 200 \text{ MHz}$ .

## Problem 2.

The SRAM block can have  $2^{32} \times 8 = 34359738368$  bits in maximum.

## Problem 3.

The approximate number of SRAM bit storage cells is  $\lfloor 10000000/6 \rfloor = 1666666$ .

## Problem 4.

SRAM cells have 6 transistors and is faster but DRAM cells have only 1 transistor and is slower. What's more, DRAM uses capacitor which discharges overtime so that it must be refreshed regularly, but SRAM needn't.

## Problem 5.

EEPROMs are erased electronically, but flash memories can be erased simultaneously.


## Problem 6.

Inputs:  $S$  (1-bit),  $P$  (1-bit),  $R$  (1-bit),  $D$  (8-bit)


Outputs:  $Q$  (8-bit)

Local Registers:  $S_0$  (1-bit),  $P_0$  (1-bit),  $s\_cnt$  (16-bit),  $p\_cnt$  (16-bit)

Memory: mem (10000x8 SRAM)

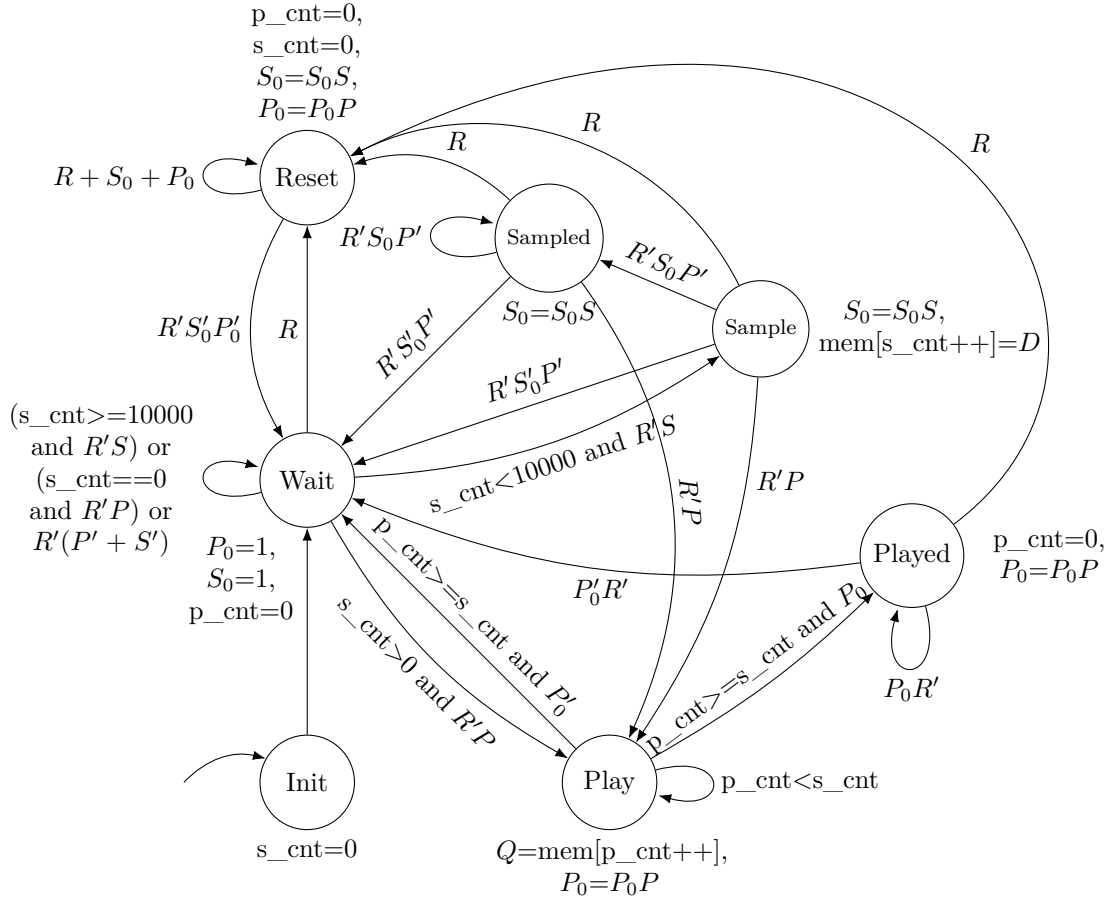

# Problem 7.

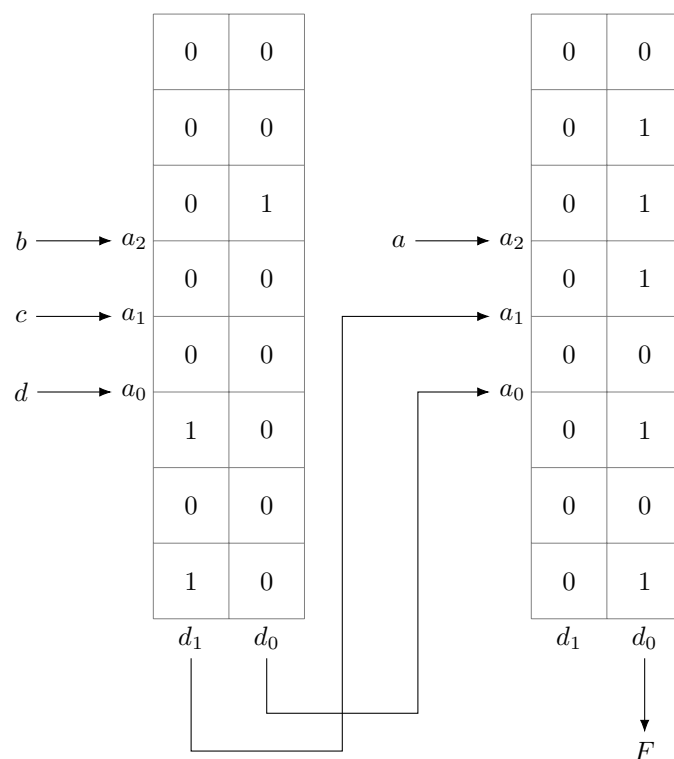

# Problem 8.

