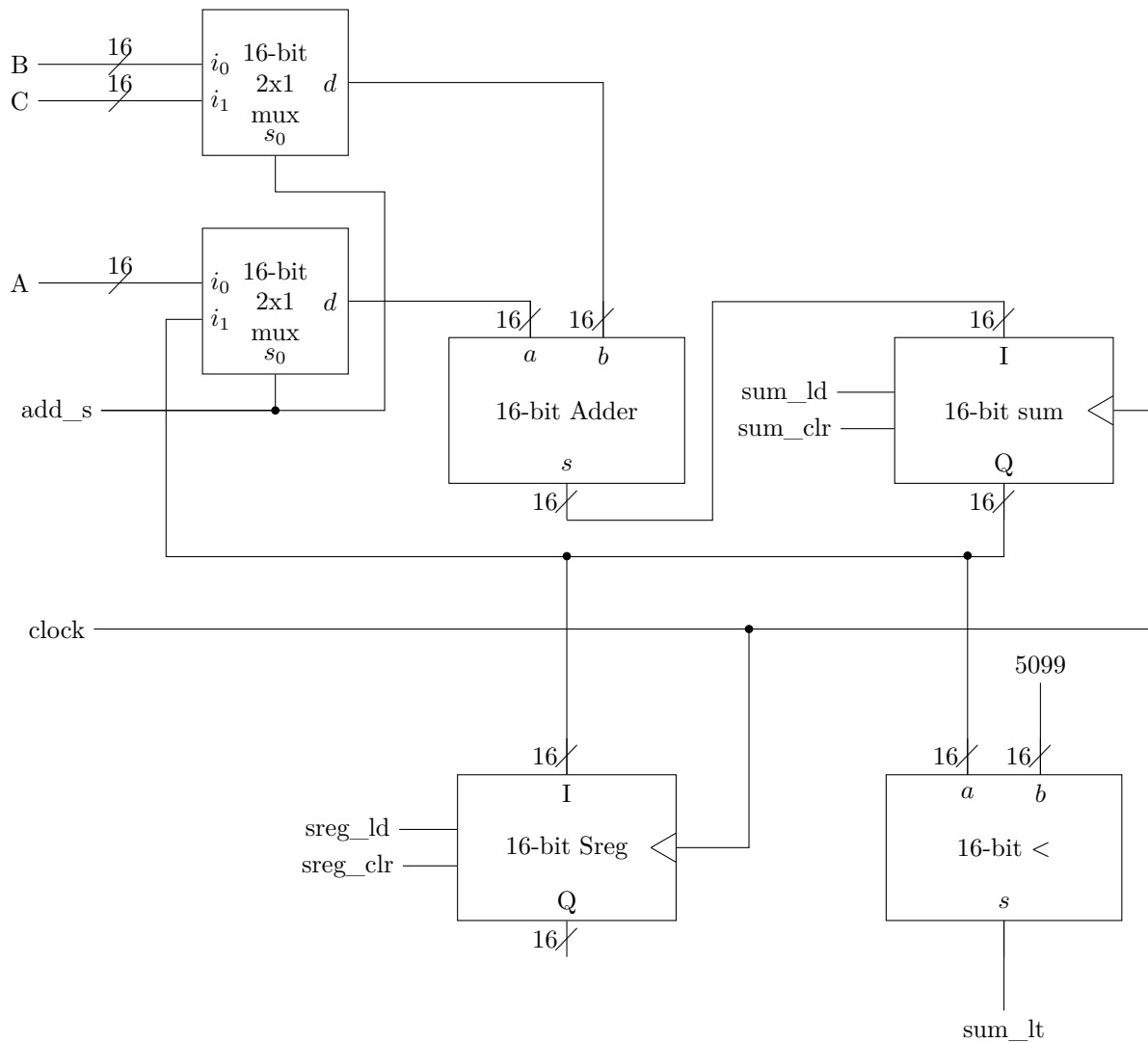


VE270 Homework 9

Liu Yihao 515370910207

Problem 1.

Inputs: A, B, C, add_s (0 for sum:=A+B and 1 for sum:=sum+C), sum_ld, sum_clr, sreg_ld, sreg_clr, clock
 Outputs: sum_lt (whether sum<5099)




Problem 2.

Step 1: HLSM Design


Inputs: clr, CT, WT

Outputs: alarm


Local registers: reg1, reg2, reg3 reg4

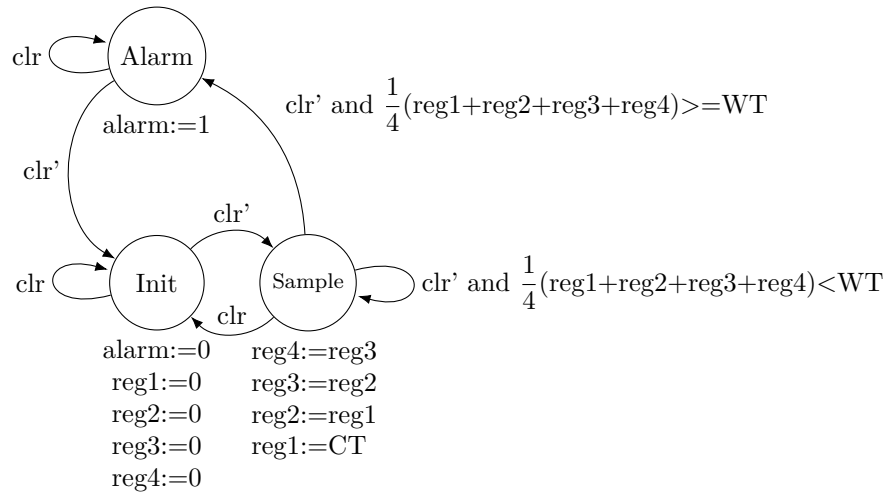

Step 2: Datapath Design

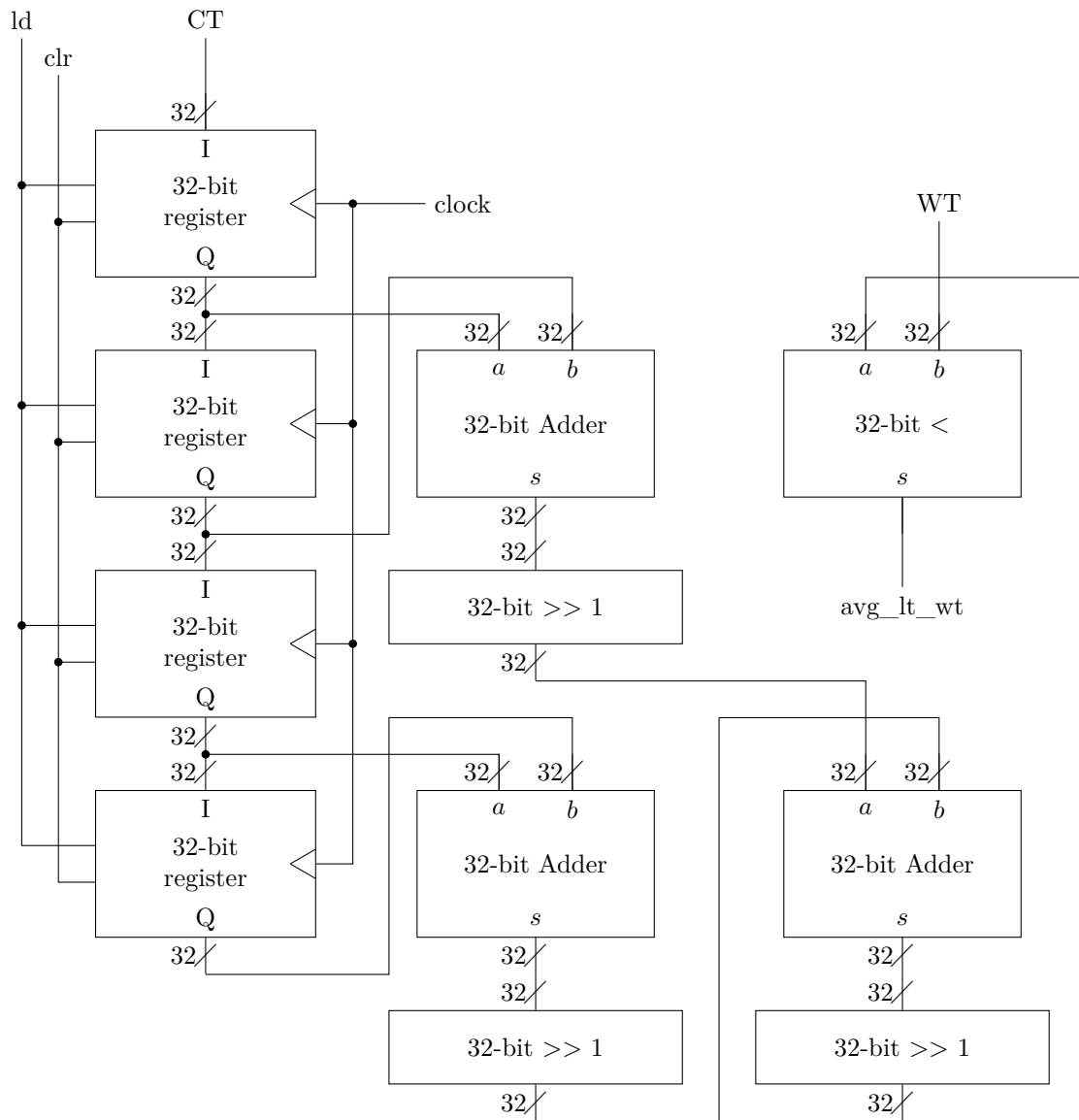

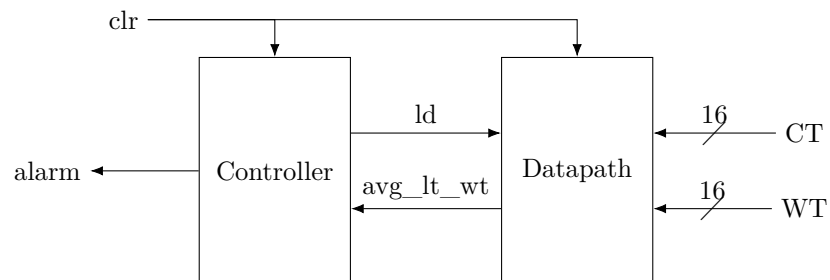
Step 3: Connect the datapath to a controller



Step 4: FSM Design

Inputs: `clr`

Outputs: `alarm`

 

Problem 3.