VE270 Homework 2

Liu Yihao 515370910207

Problem 1.

\mathbf{x}	У	$x \oplus y'$	$x' \oplus y$	$(x \oplus y)'$
0	0	1	1	1
0	1	0	0	0
1	0	0	0	0
1	1	1	1	1

$$x \oplus y' = x' \oplus y = (x \oplus y)'$$

Problem 2.

(a) $S \oplus E$

 $\mathbf{S} + \mathbf{H}'$

(c) $S \oplus EH'$

Problem 3.

$$F = a'b(c + d') + a(b' + c) + a(b + d)c$$

= $a'bc + a'bd' + ab' + ac + abc + acd$