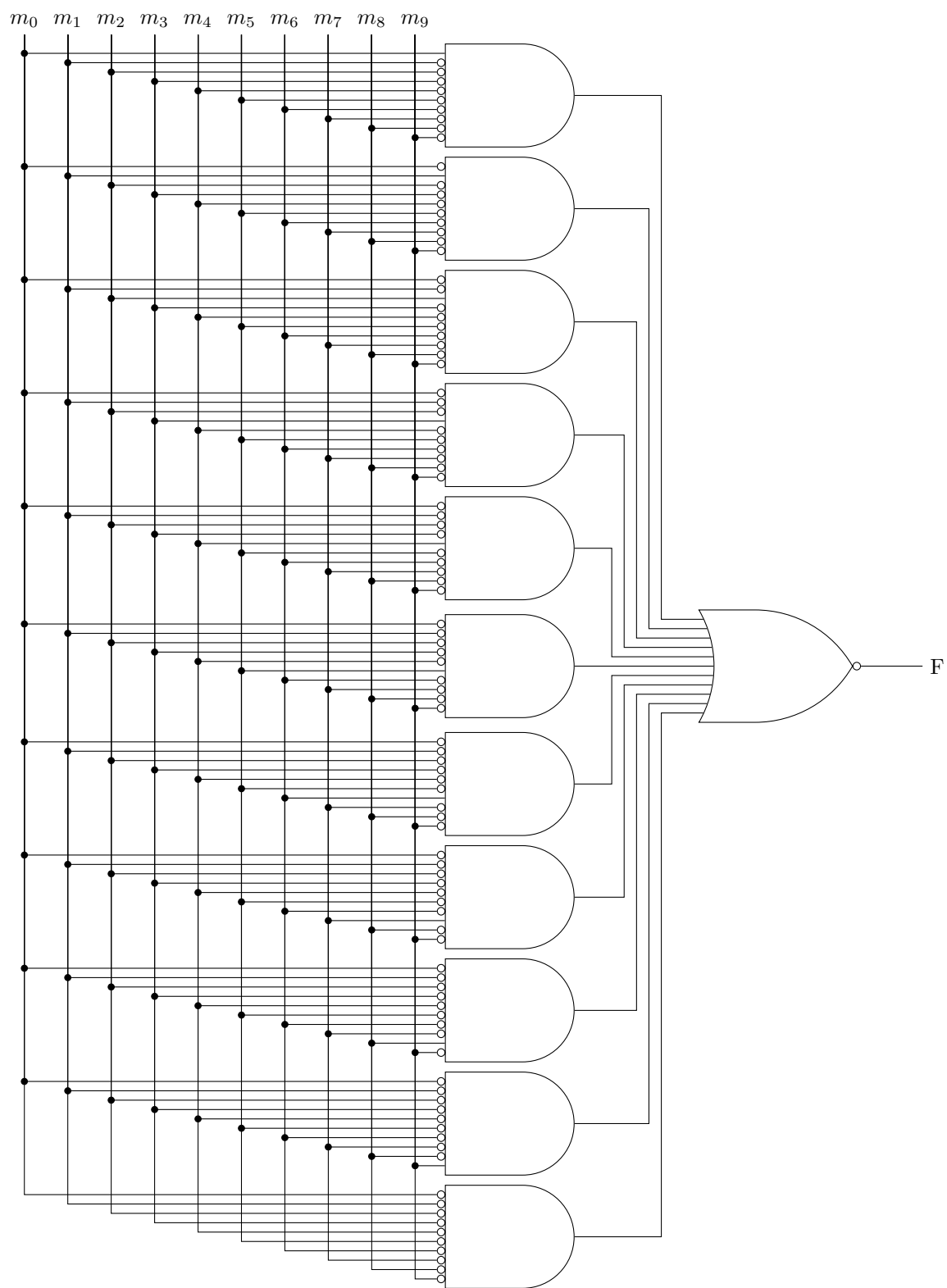


VE270 Homework 3

Liu Yihao 515370910207


Problem 1.

$$\begin{aligned} F = & (m_0 m'_1 m'_2 m'_3 m'_4 m'_5 m'_6 m'_7 m'_8 m'_9 + \\ & m'_0 m_1 m'_2 m'_3 m'_4 m'_5 m'_6 m'_7 m'_8 m'_9 + \\ & m'_0 m'_1 m_2 m'_3 m'_4 m'_5 m'_6 m'_7 m'_8 m'_9 + \\ & m'_0 m'_1 m'_2 m_3 m'_4 m'_5 m'_6 m'_7 m'_8 m'_9 + \\ & m'_0 m'_1 m'_2 m'_3 m_4 m'_5 m'_6 m'_7 m'_8 m'_9 + \\ & m'_0 m'_1 m'_2 m'_3 m'_4 m_5 m'_6 m'_7 m'_8 m'_9 + \\ & m'_0 m'_1 m'_2 m'_3 m'_4 m'_5 m_6 m'_7 m'_8 m'_9 + \\ & m'_0 m'_1 m'_2 m'_3 m'_4 m'_5 m'_6 m_7 m'_8 m'_9 + \\ & m'_0 m'_1 m'_2 m'_3 m'_4 m'_5 m'_6 m'_7 m_8 m'_9 + \\ & m'_0 m'_1 m'_2 m'_3 m'_4 m'_5 m'_6 m'_7 m'_8 m_9 + \\ & m'_0 m'_1 m'_2 m'_3 m'_4 m'_5 m'_6 m'_7 m'_8 m'_9)' \end{aligned}$$




Problem 2.

$$C = (M_0 M'_1 M'_2 M'_3 + M'_0 M_1 M'_2 M'_3 + M'_0 M'_1 M_2 M'_3 + M'_0 M'_1 M'_2 M_3 + M'_0 M_1 M'_2 M'_3)'$$

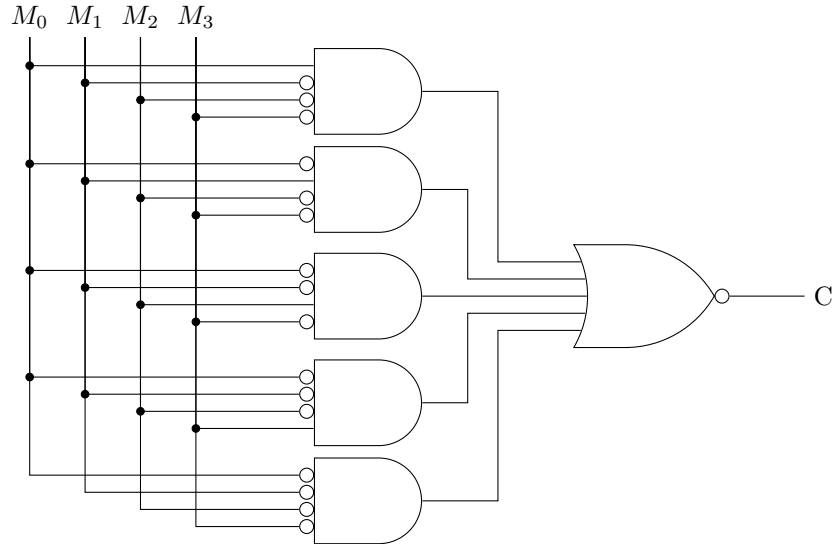


Problem 3.


Suppose m_i , $i=0,1,2,3,4$, represents the i th bit of the current tire pressure.

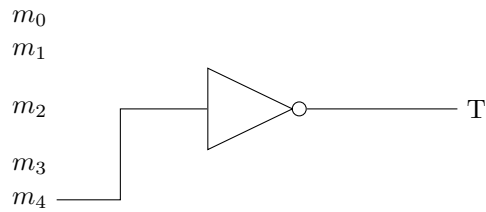


Problem 4.

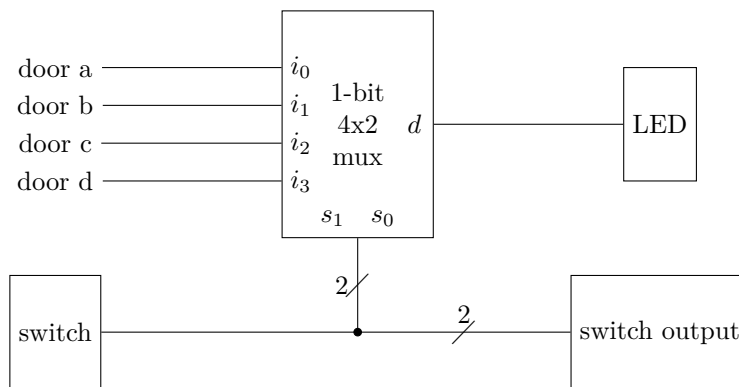


Problem 5.

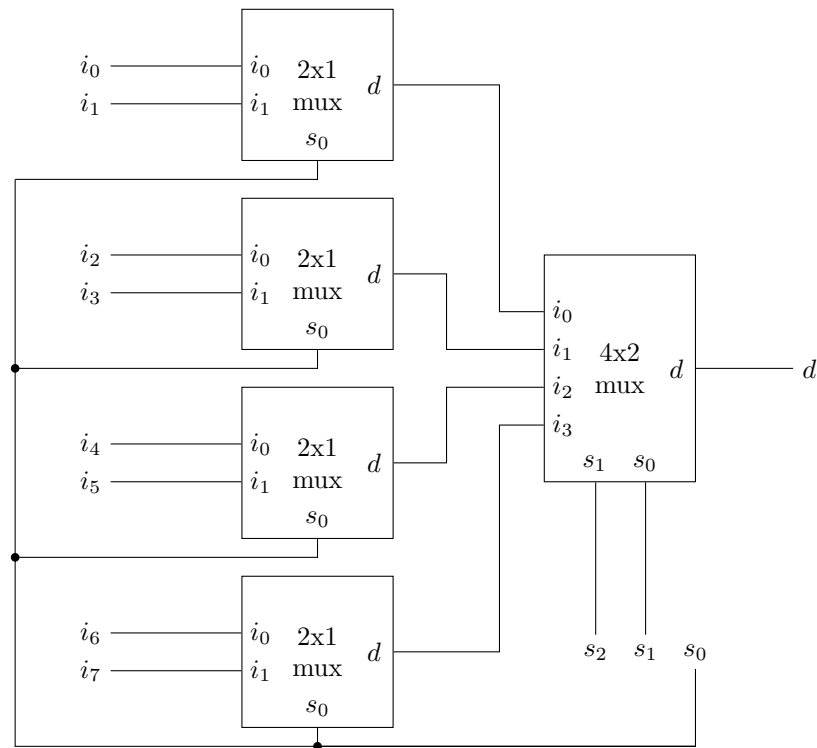


Problem 6.

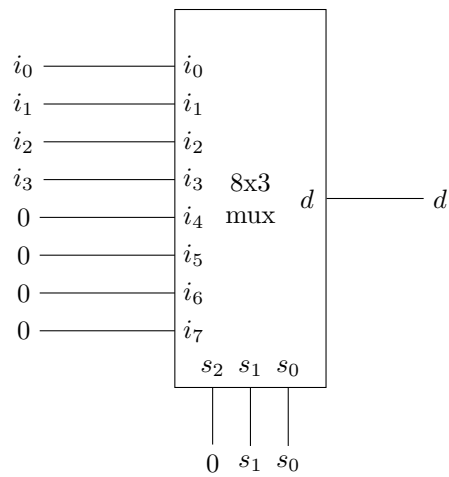

Problem 7.

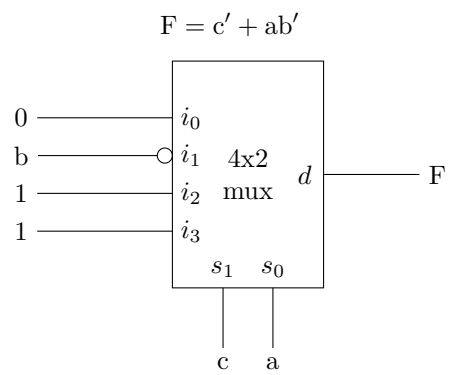


Problem 8.

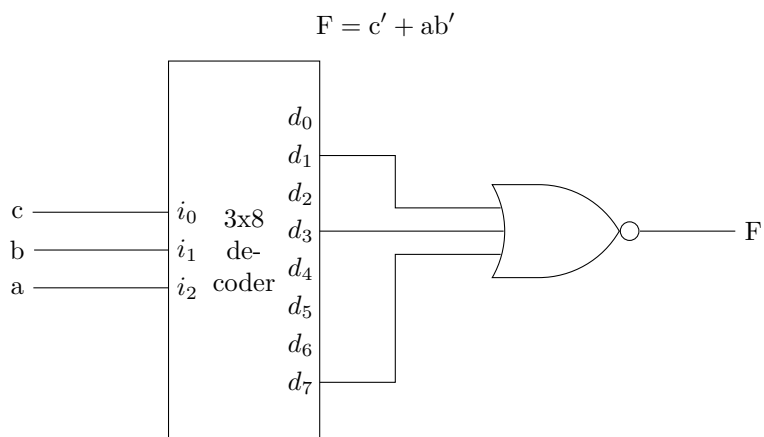


Problem 9.


The inner design of 8-bit and gate:

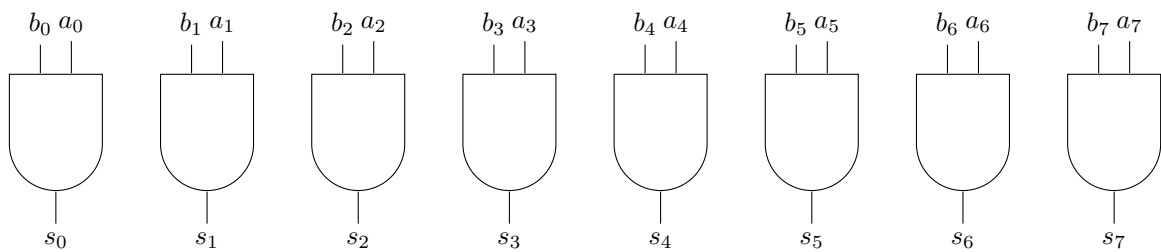


The inner design of 8-bit or gate:

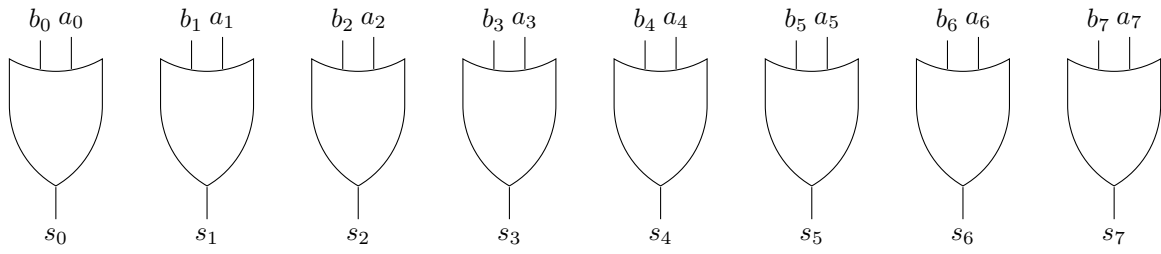


The inner design of 8-bit xor gate:

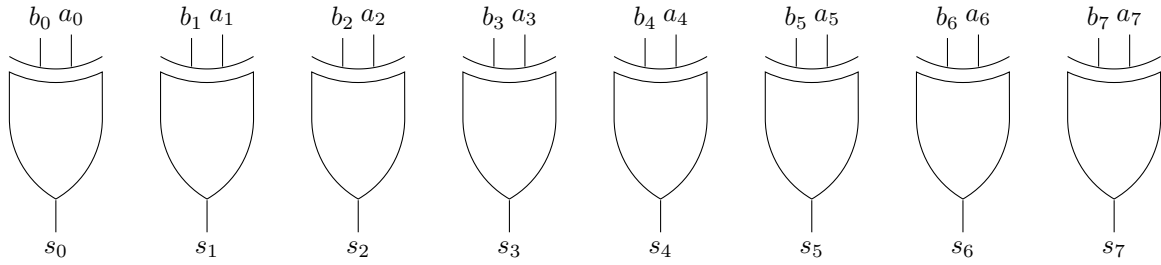


The inner design of 8-bit not gate:

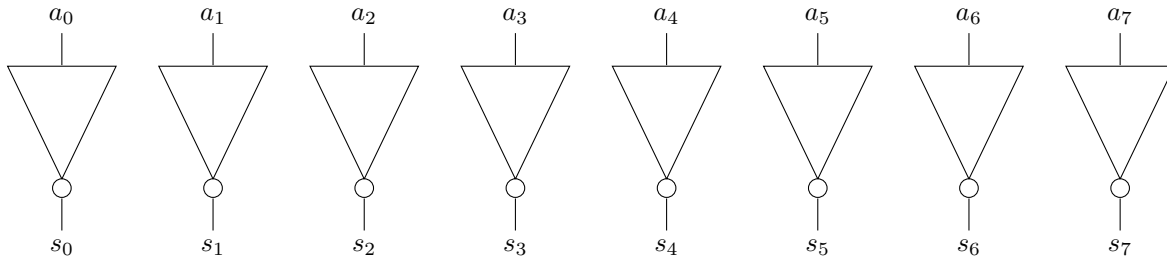

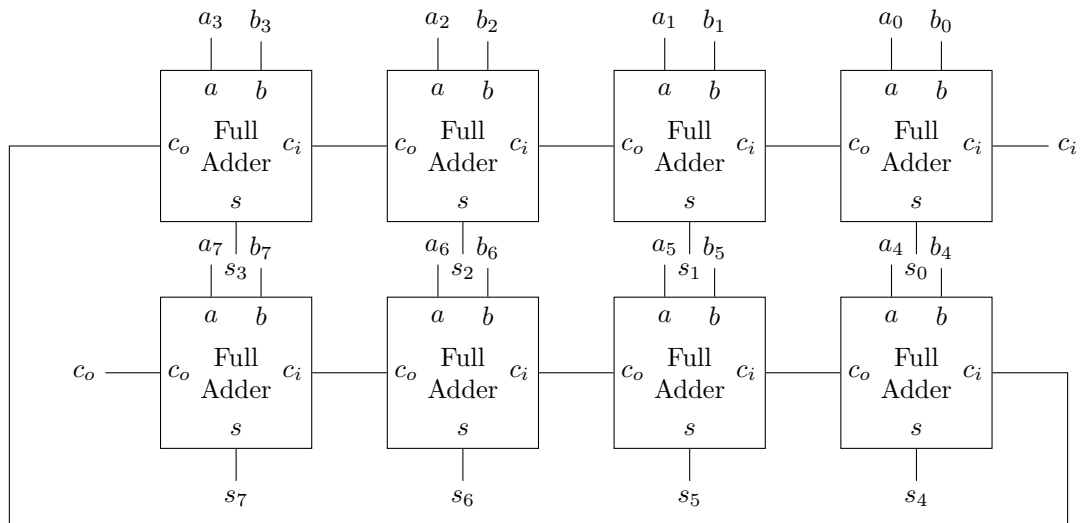The inner design of 8-bit Carry Ripple Adder:



The design of ALU:

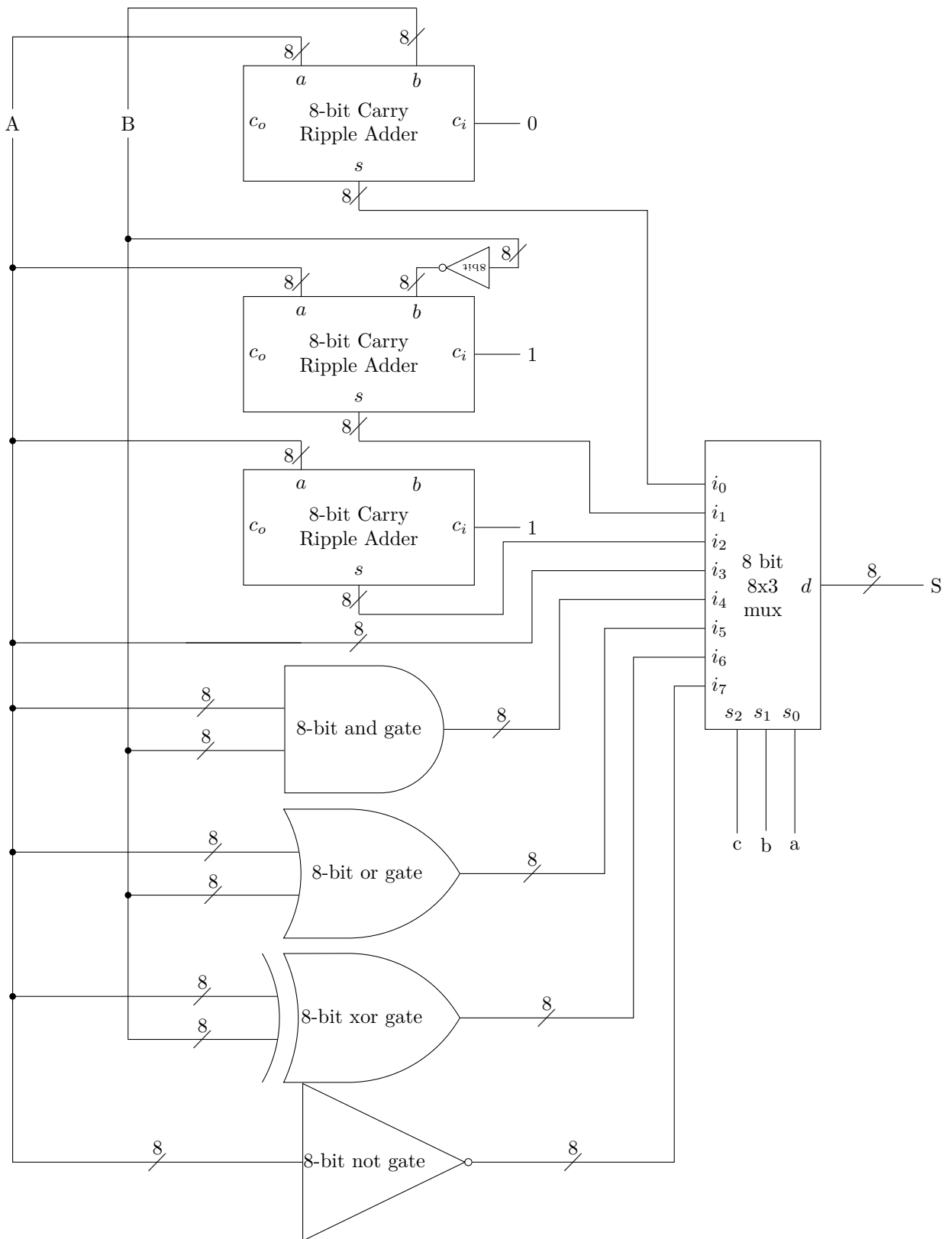

Problem 10.

$$t_a = t_b = 0.5 + 1 + 0.5 + 0.75 + 0.5 + 1 + 0.5 = 4.75 \text{ ns}$$

$$t_c = 0.5 + 0.75 + 0.5 + 1 + 0.5 = 3.25 \text{ ns}$$

One of the critical paths is shown below.

