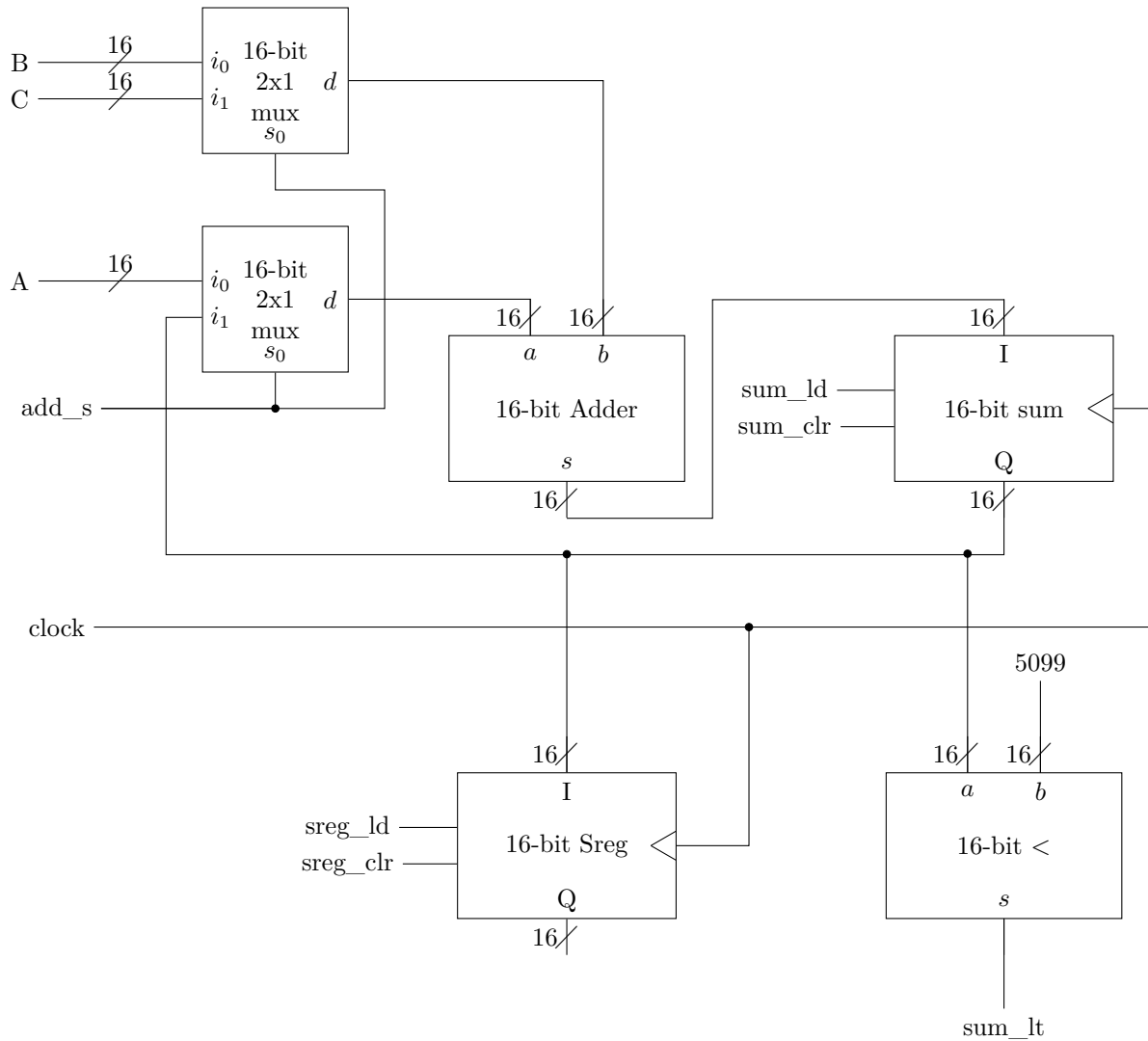


VE270 Homework 9

Liu Yihao 515370910207

Problem 1.

Inputs: A (16 bits), B (16 bits), C (16 bits), add_s (bit, 0 for sum:=A+B and 1 for sum:=sum+C),
sum_ld (bit), sum_clr (bit), sreg_ld (bit), sreg_clr (bit), clock (bit)
Outputs: sum_lt (bit, whether sum<5099)




Problem 2.

Step 1: HLSM Design


Inputs: clr (bit), CT (32 bits), WT (32 bits)

Outputs: alarm (bit)

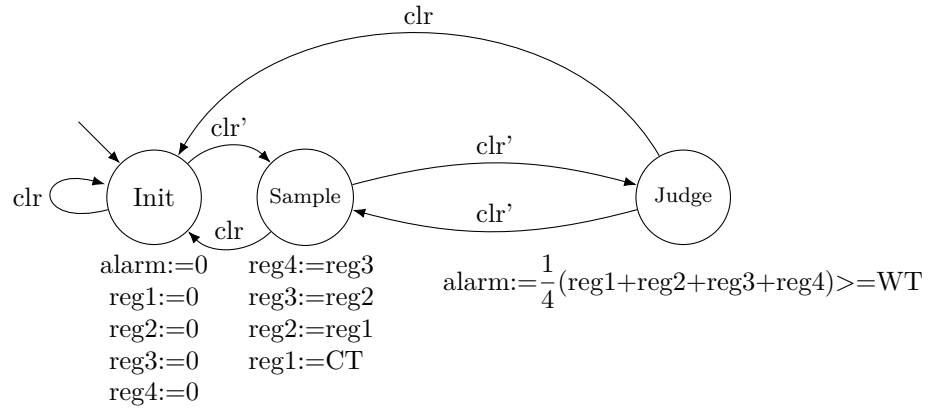
Local registers: reg1, reg2, reg3, reg4 (all 32 bits)



Step 2: Datapath Design

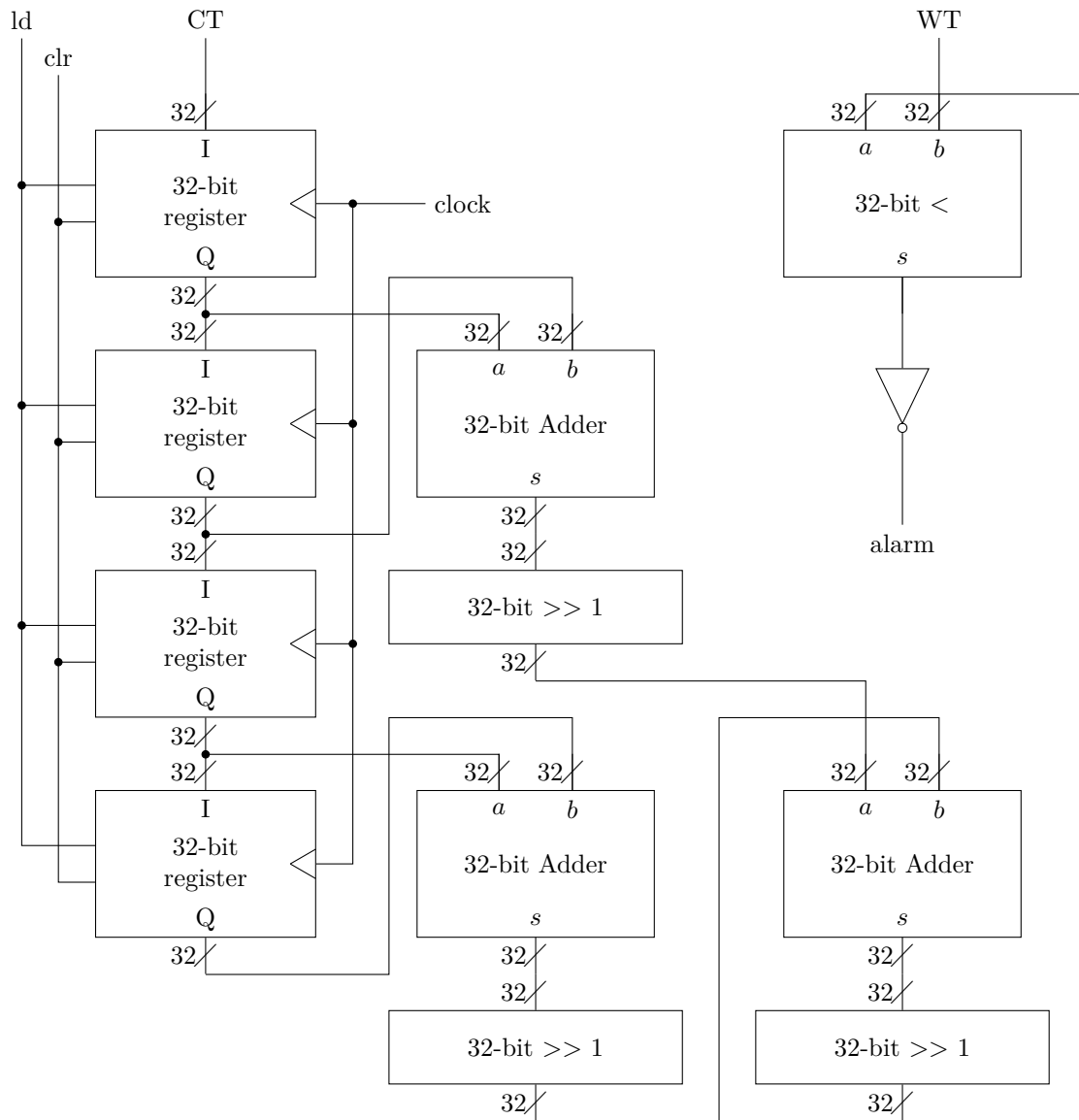

 
Step 3: Connect the datapath to a controller



Step 4: FSM Design

Inputs: clr


Outputs: ld

 

Problem 3.

Inputs: i_lt16

Outputs: i_ld , i_clr , s_ld , s_clr , a_ld , a_clr , avg_ld , avg_clr

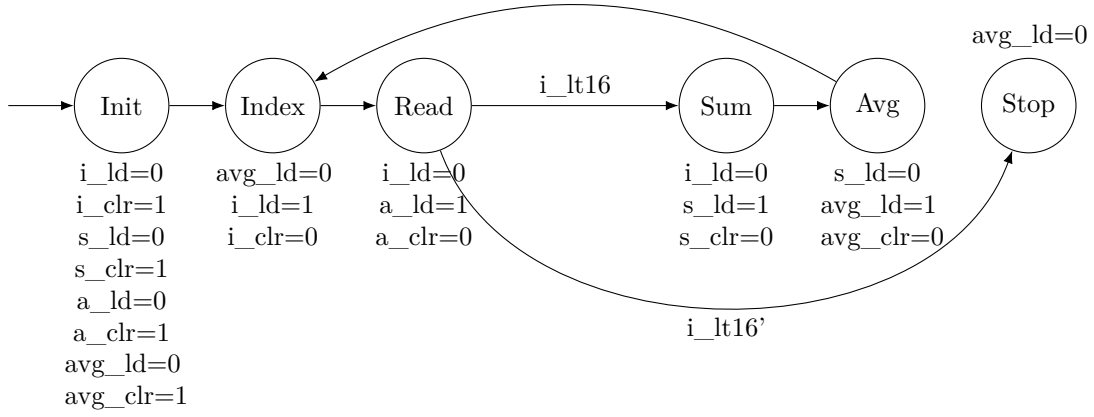


Problem 4.

Step 1: HLSM Design


Inputs: Valid (bit), Data_in (bit)

Outputs: RxReg (8 bits)


Local registers: i (3 bits), r (8 bits)

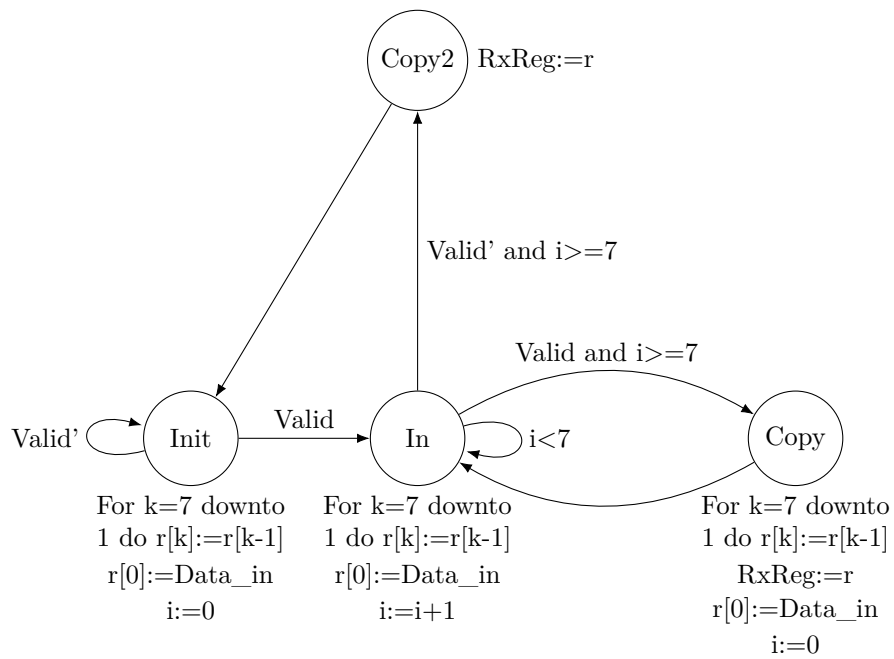

Step 2: Datapath Design

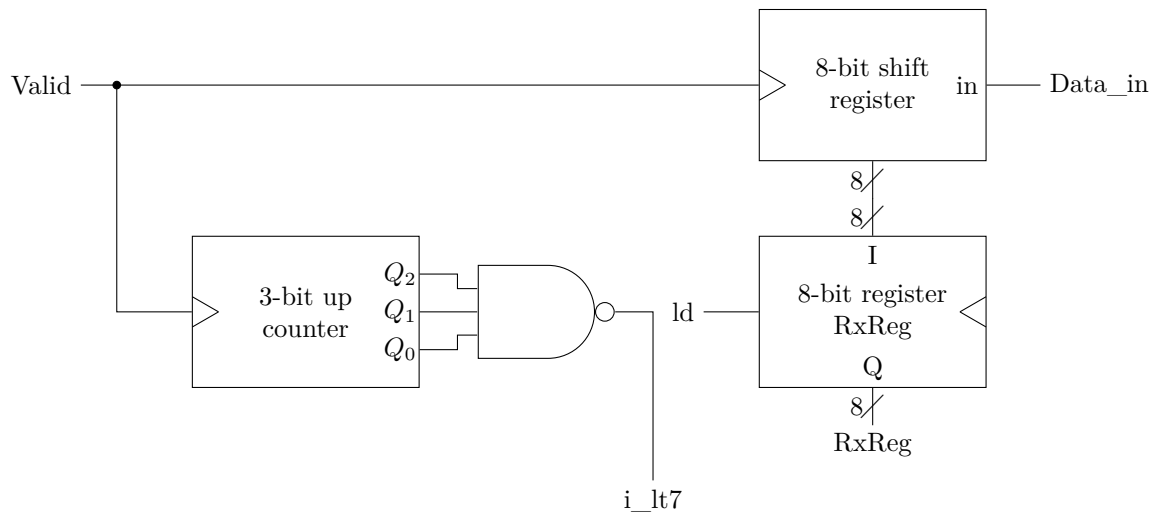

 Step 3: Connect the datapath to a controller



Step 4: FSM Design
 Inputs: Valid, i_lt7
 Outputs: ld

