



University of Michigan

—◆交大密西根学院◆—  
UM-SJTU Joint Institute



Shanghai Jiao Tong University

## Lab Report

# 2

UM-SJTU Joint Institute

---

## Ve270 Introduction to Logic Design

by

Liu Yihao 515370910207

Ma ShiYao 515370910157

Date: 2017-06-06

## Design of an SSD Driver



University of Michigan

◆ 交大密西根学院 ◆

UM-SJTU Joint Institute



Shanghai Jiao Tong University

## 1 Objectives

To design a Seven-Segment Display (SSD) driver using Xilinx ISE, and to implement the circuit in an FPGA chip.

## 2 Problem Definition

To form SSD as a digit-display system. By inputting 4-bit binary number, seven cathode will receive a 7-bit binary digit for the seven segments of the LED, then the corresponding parts of the LED will illuminate to form the correct decimal digit. When the cathode receives a “0” and the anode receives an “1”, the LED is turned on. The input of this system is a 4-bit binary number, the output is the corresponding decimal digit displayed by LED. As an example, when the driver receives “0101” as input, the decimal number “5” will be displayed.

## 3 System Partitioning

1. Switch and driver: switches and driver are used to input 4-bit binary digit signal. By toggling different switches, the driver will receive the binary digit inputted, then convert it to anodes and cathodes.
2. Anodes and cathodes: used for receiving the signal from driver, and controlling the LED segments.
3. LED segments: to receive the signal converted from the anodes and cathodes, and illuminate to form the corresponding decimal digit.

## 4 Design Entry

The overall truth table was shown in Table 1.

Input	Outputs(LED segments)						
	CA	CB	CC	CD	CE	CF	CG
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	1	0	1	1

Table 1: Overall truth table

First, we designed some macros to translate different inputs into numbers, for example, the schematics design and symbol for input number 1 (0001) was shown in Figure 1.



University of Michigan

◆ 交大密西根学院 ◆

UM-SJTU Joint Institute



Shanghai Jiao Tong University

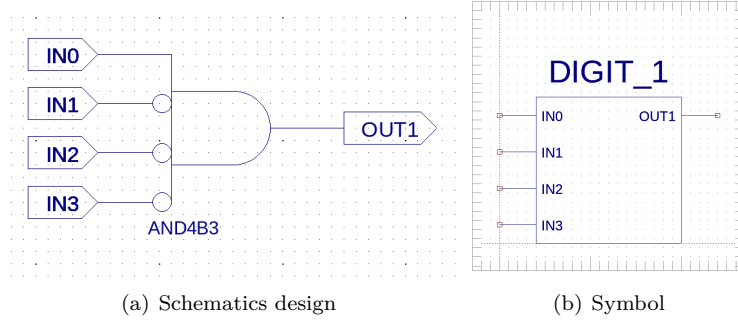


Figure 1: Schematics design and symbol for input number 1

According to this truth table, we designed a circuit for each input segment, shown in Figure 2.

At last, we build the symbols for the seven input segments and designed a final circuit of SSD, shown in Figure 4.



University of Michigan

◆ 交大密西根学院 ◆  
UM-SJTU Joint Institute



Shanghai Jiao Tong University

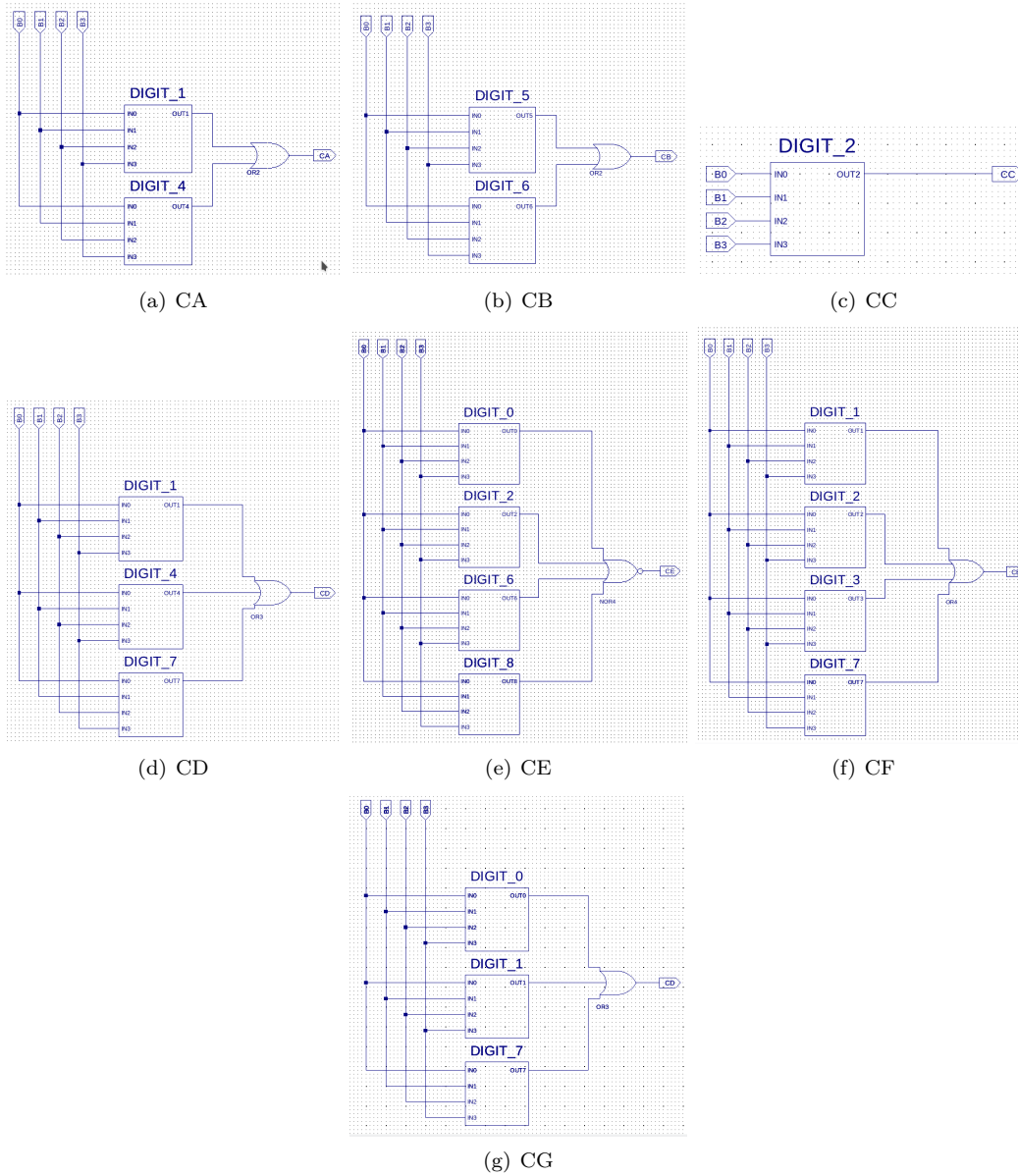


Figure 2: Schematics design for input segments



University of Michigan



Shanghai Jiao Tong University

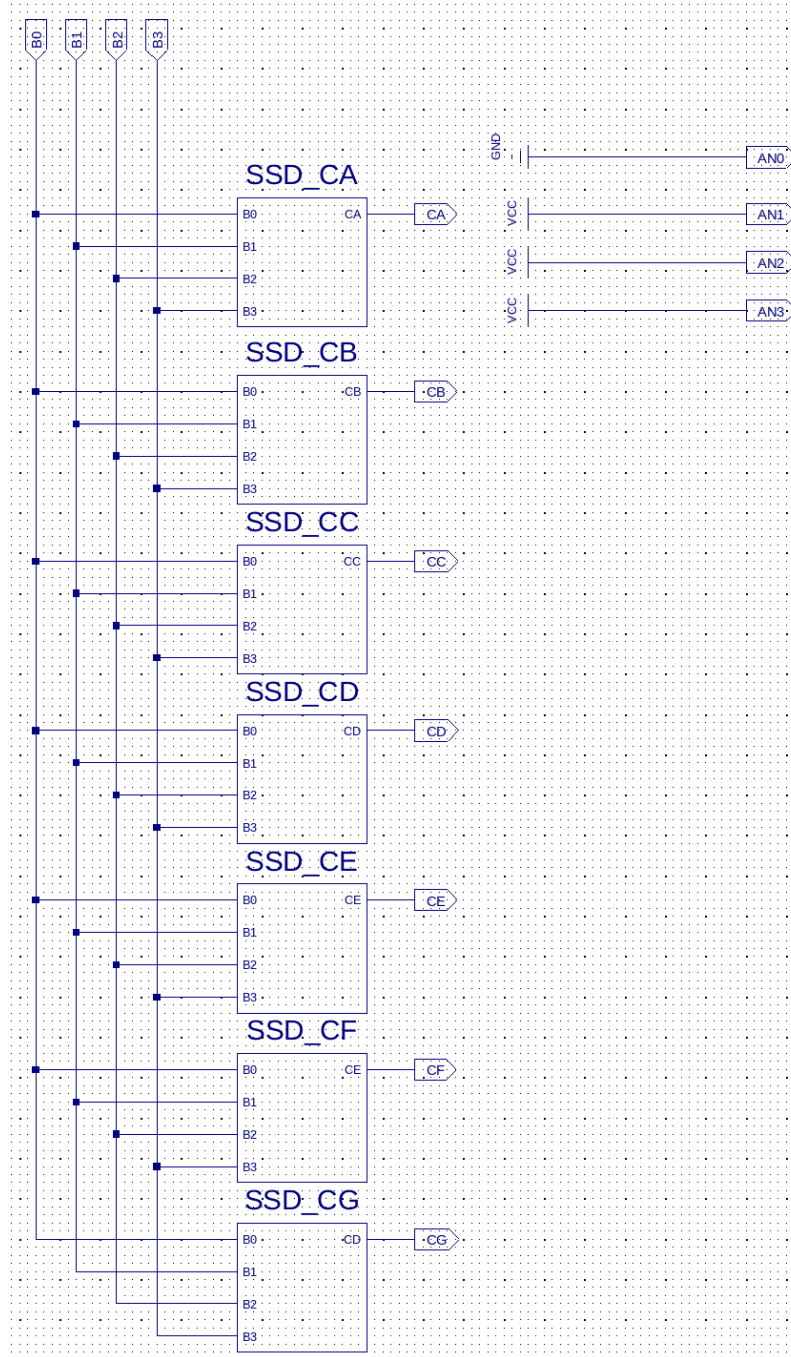


Figure 3: Schematics design for SSD



University of Michigan

◆ 交大密西根学院 ◆

UM-SJTU Joint Institute



Shanghai Jiao Tong University

## 5 Test Plan

Test content	Test method
CA	Input signal that needs corresponding LED segment to illuminate, then observe if it illuminates. If it illuminates when corresponding signal inputted, this subsystem passes the test; otherwise it fails.
CB	
CC	
CD	
CE	
CF	
CG	
The overall system	Input every kind of the 4-bit binary digit signal: 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001, then observe if LED displays the corresponding decimal digit: 1, 2, 3, 4, 5, 6, 7, 8, 9. If so, the system passes the test; otherwise it fails.

## 6 Simulation Results

We simulated the result of the overall system with input values B0,B1,B2,B3 as 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001. The result was shown in Figure ??.

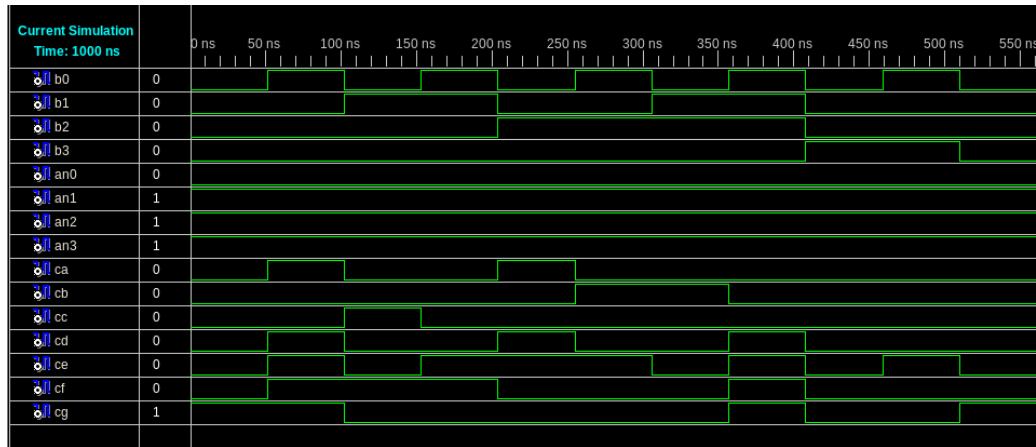


Figure 4: Simulation of SSD

We found the values in the simulation identical to the truth table we built as Table 1, which proved that our design was right.



University of Michigan

—◆交大密西根学院◆—  
UM-SJTU Joint Institute



Shanghai Jiao Tong University

## 7 Conclusion

In this lab, we successfully finished it finally, but we still met some problems in the process. in our first try, we found the LED segments that should be off turned on, but the parts should be on did not illuminate. by testing our circuits and simulation, we found that we mistaken cathode and anode in our previous version. by changing anode and cathode, the whole system runs well.it is a good practice for us to build a logic circuit.

## 8 Appendix

The schematics of our design had been submitted to canvas before.