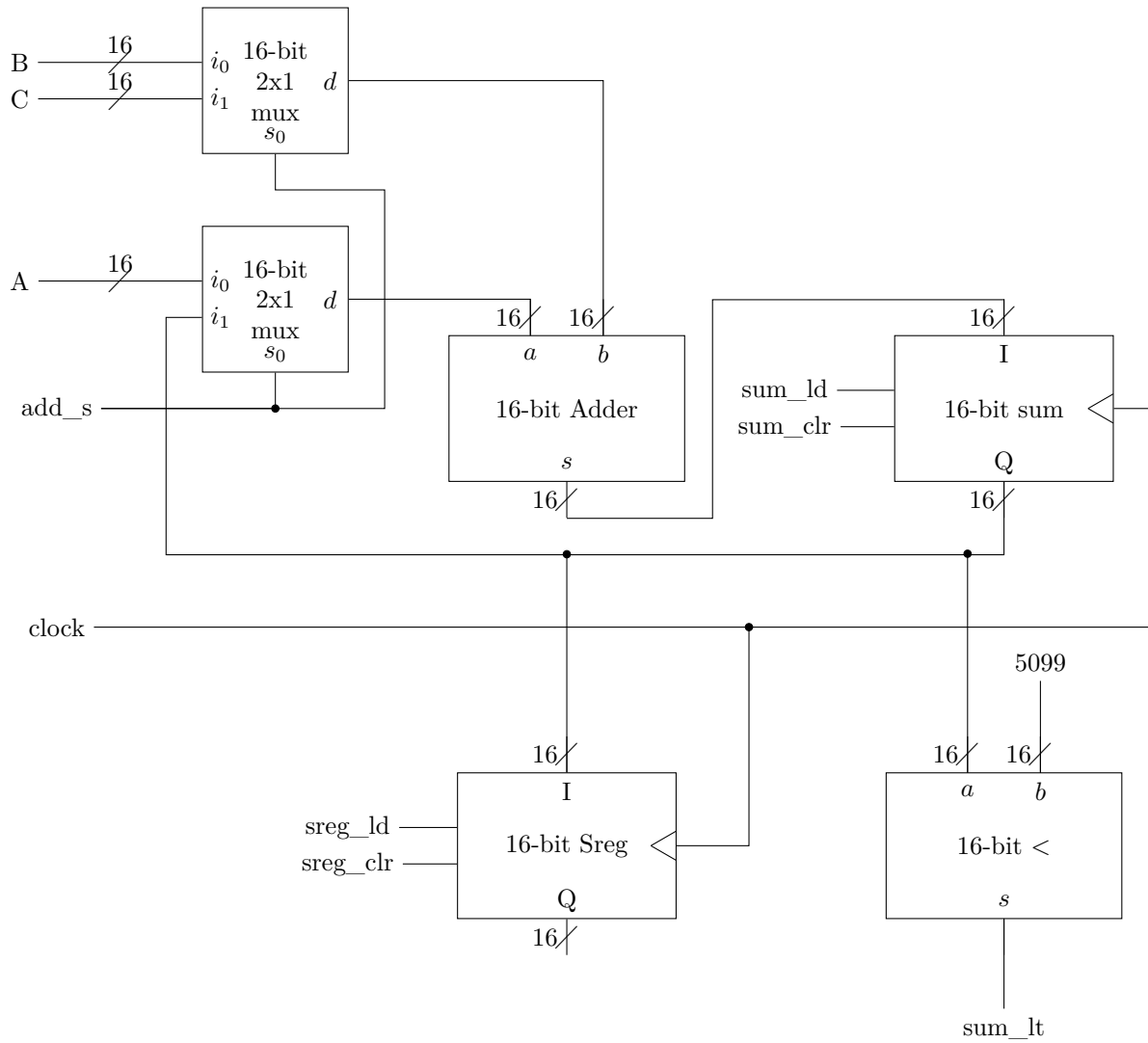


VE270 Homework 9

Liu Yihao 515370910207

Problem 1.

Inputs: A, B, C, add_s (0 for sum:=A+B and 1 for sum:=sum+C), sum_ld, sum_clr, sreg_ld, sreg_clr, clock
Outputs: sum_lt (whether sum<5099)




Problem 2.

Step 1: HLSM Design


Inputs: clr, CT, WT

Outputs: alarm


Local registers: reg1, reg2, reg3 reg4

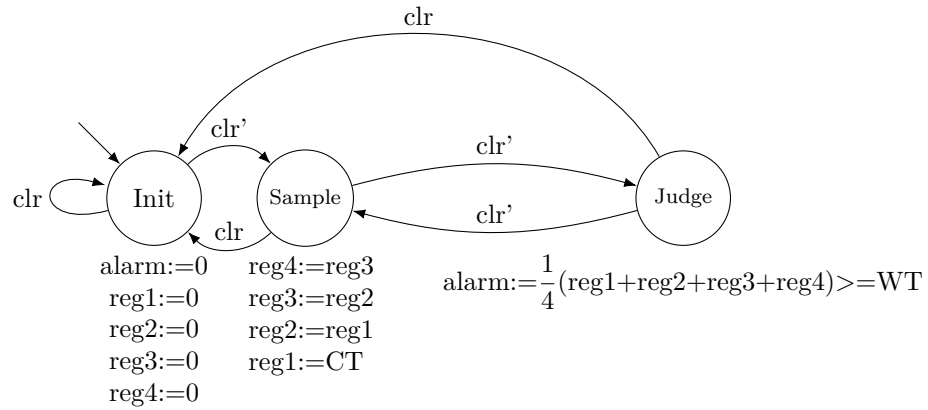

Step 2: Datapath Design

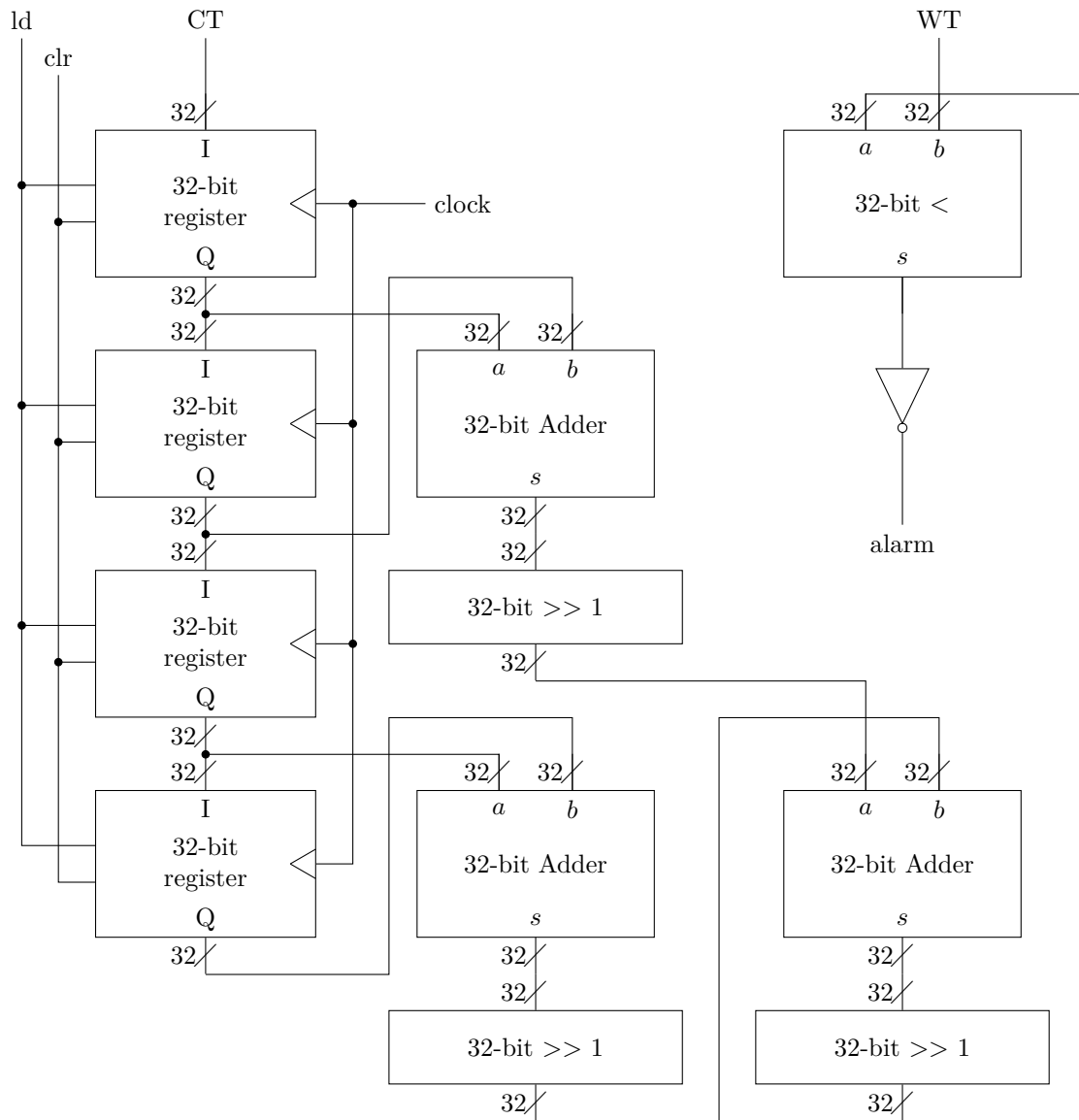

 
Step 3: Connect the datapath to a controller



Step 4: FSM Design

Inputs: clr


Outputs: ld

 

Problem 3.

Inputs: i_lt16

Outputs: i_ld , i_clr , s_ld , s_clr , a_ld , a_clr , avg_ld , avg_clr

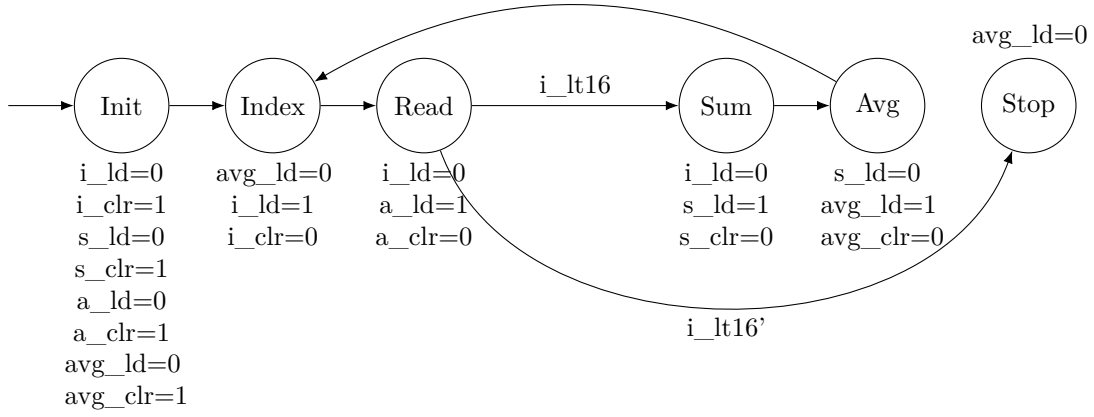

Problem 4.

Step 1: HLSD Design

Inputs: Valid (bit), Data_in (bit)

Outputs: RxReg (8 bits)

Local registers: i (3 bits), r (8 bits)

